

ECE 553: TESTING AND TESTABLE DESIGN OF DIGITAL SYSTEMS

Sequential circuit testing -
Checking experiment approach

10/22/2006

3

Overview

- Motivation and introduction
- Model and fault model
- Theory
- Checking experiment design
- Limitations of the method
- Summary

10/22/2006

2

Motivation and Introduction

- Ref: F.C. Hennie “Fault detection experiments for sequential circuits”, 5th annual symposium on switching and automata theory, 1964.
- Motivation
 - Test generation at higher level of abstraction in which only the function of the circuit is known but the implementation (structure) is not known

10/22/2006

3

An example

- Consider testing a 4-bit ALU
 - We need not know the structure – we can determine the number of inputs and outputs. If the number is small we can test the circuit exhaustively.
 - Can such a technique be used for sequential circuits, even if it is fairly small, such as a small finite state machine. Such FSMs exist often in practice (embedded controllers are good examples of such FSMs).
 - Derivation of tests for such circuits is of interest for the following two reasons
 - Need not worry about the realization and underlying technology
 - Such tests can also be used for validation and verification

10/22/2006

4

Sequential circuit model

- Two ways to express a state machine
 - State table
 - State diagram
 - $M = (Q, I, O, NS, OU)$
 - Q = set of states
 - I = set of inputs from an input alphabet
 - O = set of outputs from an output alphabet
 - NS = next state function
 - OU = output function

10/22/2006

5

Fault model

- Two formulations of the test problem
 - Given the behavior of the circuit (such as state table), verify the behavior by applying the inputs and observing the outputs. Object is to find a sequence of inputs that will verify the behavior
 - Given a sequence of inputs and outputs, construct a state machine that will behave as specified by the input/output sequence
- The above two problems have similarities but we will address the first of the two problems

10/22/2006

6

Fault model

- Assumptions about the faults
 - Number of states in the FSM are known or these are upperbounded
 - No fault causes an increase in the number of states or increase beyond the upperbound
- We will also limit our discussion to a class of FSMs that have some special properties. These properties are defined in the “theory” section of the discussion

10/22/2006 7

Theory

- Strongly connected machine/circuit: every state is reachable from every other state
 - There are no “source” or “sink” states
- An example FSM – strongly connected?

PS	x = 0	x = 1
A	C/0	A/0
B	B/1	D/0
C	A/0	B/0
D	B/1	C/0

10/22/2006 8

Theory (contd.)

- Synchronizing sequence

Application of this sequence takes the machine to a known state (final state), irrespective of the start state (initial state) of the circuit

PS	x = 0	x = 1
A	C/0	A/0
B	B/1	D/0
C	A/0	B/0
D	B/1	C/0

- Synchronizing tree – see next slide

10/22/2006 9

Theory (contd.)

- Synchronizing tree
- Ambiguity – states the circuit may be in
- Example:
 - initial ambiguity (ABCD)
 - after an application of 0 the ambiguity is (ABC)
- SS = 0 1 0 1 0 (Final state = B)

PS	x = 0	x = 1
A	C/0	A/0
B	B/1	D/0
C	A/0	B/0
D	B/1	C/0

10/22/2006 10

Theory (contd.)

- Homing sequence – application of this sequence and observation of outputs can determine the final state of the circuit
- Distinguishing sequence – application of this sequence and the observation of outputs and determine the initial (start) state of the circuit
 - Clearly this can also determine the final state of the circuit

10/22/2006 11

Theory (contd.)

- Homing sequence
 - Construct a homing tree
 - 010 is a homing sequence
 - If output 000 – final state is C
 - If output 101 – final state is B
- Distinguishing sequence –
 - Construct a distinguishing tree
 - This machine does not have a DS
- Transfer sequence –
 - a sequence, T_{ij} , that will take the machine from state i to j

PS	x = 0	x = 1
A	C/0	A/0
B	B/1	D/0
C	A/0	B/0
D	B/1	C/0

10/22/2006 12

Theory (contd.)

- Example:
- SS ?
- HS ?
- DS = 100

PS	x = 0	x = 1
A	C/0	D/1
B	C/0	A/1
C	A/1	B/0
D	B/0	C/1

st	output	st
A	1 0 0	C
B	1 0 1	A
C	0 0 1	A
D	1 1 0	C

10/22/2006
13

Checking experiment design

- Two part sequence
 - Part 1: verify that the FSM has n states
 - Check that there are n distinct states
 - Part 2: verify that all transitions from every state are correct
 - Apply one input at a time and check the output and the state of the circuit

10/22/2006
14

Checking experiment design (contd.)

- Checking sequence construction
 - Apply SS and take the circuit to a known state
 - Repeat for each state
 - (known state) DS (transfer to another, different, state)
 - DS is used to verify the known state
 - Repeat of each state and every input
 - (known state) input DS (transfer to a known state)
 - verify output when input is applied
 - DS is used to verify that the transition was indeed correct

10/22/2006
15

Checking experiment design (contd.)

- An example

PS	x = 0	x = 1
A	C/0	D/1
B	C/0	A/1
C	A/1	B/0
D	B/0	C/1

- Phase 1: SS T_{CA} DS T_{CB} DS T_{AC} DS T_{AD} DS
 C C A A C
- Phase 2: T_{CA} 0 DS T_{AA} 1 DS ...
 check null check
 output output

10/22/2006
16

Checking experiment design (contd.)

- Checking sequence – reducing sequence length
 - States need not be verified in the order we want them, they can be verified as they appear while designing the sequence
 - Phases 1 and 2 can be overlapped
 - Overlap parts of sequences where ever possible
 - If there is more than one DS, these can be integrated with in the design of sequence

10/22/2006
17

Limitations of the method

- Assumptions are very restrictive and limit the application of the method
- Machine do not have SS, DS, etc. require more complex algorithms
- Length of the sequence can be very long
 - SS can be as long as O(n³)
 - The known best bound is n(n+1)(n-1)/6
 - TS can be no longer than length n
 - DS – this can be very long in theory
 - (n-1)nⁿ
 - Hence total sequence length can be O(2^{kn}), where k is the number of flip-flops and n=2^k

10/22/2006
18

Summary

- Need for functional testing methods for sequential circuits
- Described a fault model for functional faults in FSMs
- Developed theoretical foundation for FSM testing
- Design of test sequence
- Limitations of the method

10/22/2006

19