

# A Globally-Asynchronous Locally-Synchronous VLSI Circuit for the SAFER Cryptoalgorithm

T.Villiger, J.Muttersbach, H.Kaeslin, N.Felber, W.Fichtner  
Integrated Systems Laboratory, Swiss Federal Institute of Technology

ACiD-WG Workshop, Neuchatel, Switzerland

Funded by: Infineon Technologies, Germany  
Philips Semiconductors Zürich, Switzerland  
Commission for Technology and Innovation, Switzerland


# Outline

---

- GALS principle
- GALS building blocks
- Data channels
- SAFER cryptoalgorithm
- Architecture of the cryptochip
- Design flow
- Results
- Conclusion, Future work
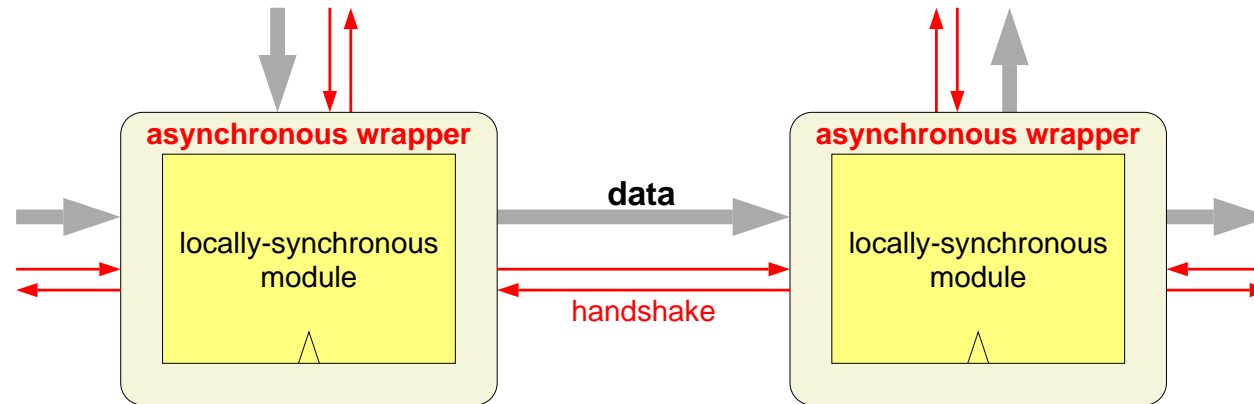
# GALS Principle


- Locally-synchronous (LS) modules perform all functionality
- Data are transferred in self-timed manner between LS modules



Benefits:

- Facilitates clocking of SOCs
- Modularity enhances optimization and re-use of LS blocks
- Provides a hook for low-power operation
- Natural inclusion of totally asynchronous modules



# The asynchronous wrapper

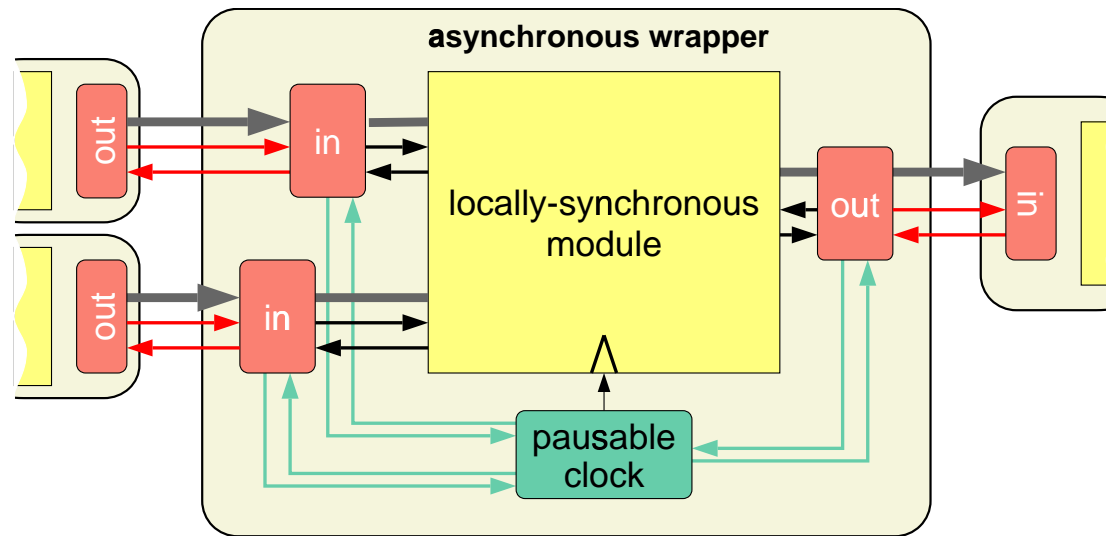

- Asynchronous port controllers allow for fast handshake processing
- Metastability of data is **prevented** by pausing the clock
- No extra latency (synchronizers, FIFOs. . . ) introduced
- Wrapper shall be assembled from predesigned elements

 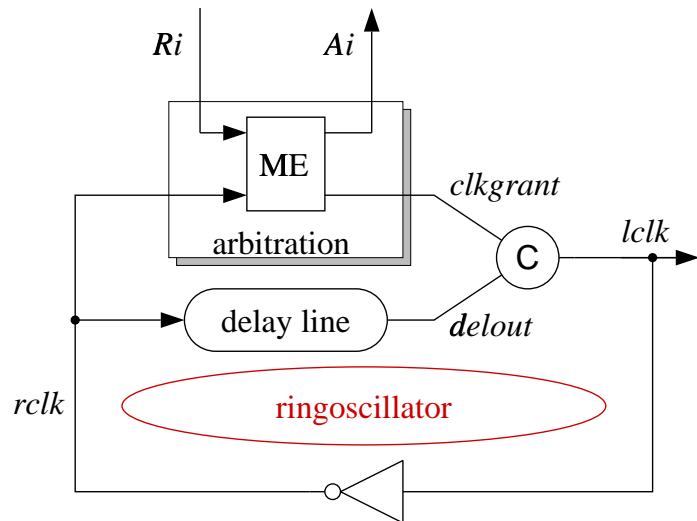
# Pausable clock generation

- Ring oscillator for local clock generation
- Arbitration with Mutual Exclusion (ME) elements
- Programmable delayline




# Delayline and Arbitration

## Principle of delayline using slices

 

- every slice can bypass rest of delayline
- delay adjustable over a wide range
- small delay increment ( $\approx 350\text{ps}$  per slice with  $0.25\mu\text{m}$  technology)

## Multiple Arbitration block

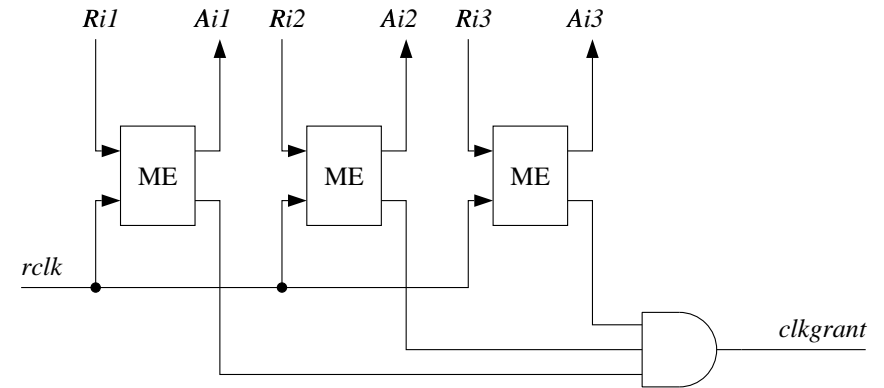


- safely arbitrates between incoming requests and rising edges on rclk
- row of mutual exclusion elements
- scales linearly to multiple ports

# GALS building blocks

---

- Port controller responsible for managing all data transfers
- Each unit is captured by a structural VHDL description
- Asynchronous port controllers achieve cycle times less than 350ps
  
- A **Poll-type** ports ask for clock stretching only to prevent metastability and ensure data correctness: “proceed while waiting”
- **Demand-type** ports also ensure data integrity but stop the local clock as soon as they are enabled: “sleep while waiting”
- **ROM (LUT) port:** Interface at the ROM port is just a fake delay between  $R_p$  and  $A_p$  matching the data delay
- **RAM access:** Essentially a Demand-Out port with bidirectional data transfer (two data vectors in opposite direction controlled by a common handshake pair)

# D-input port

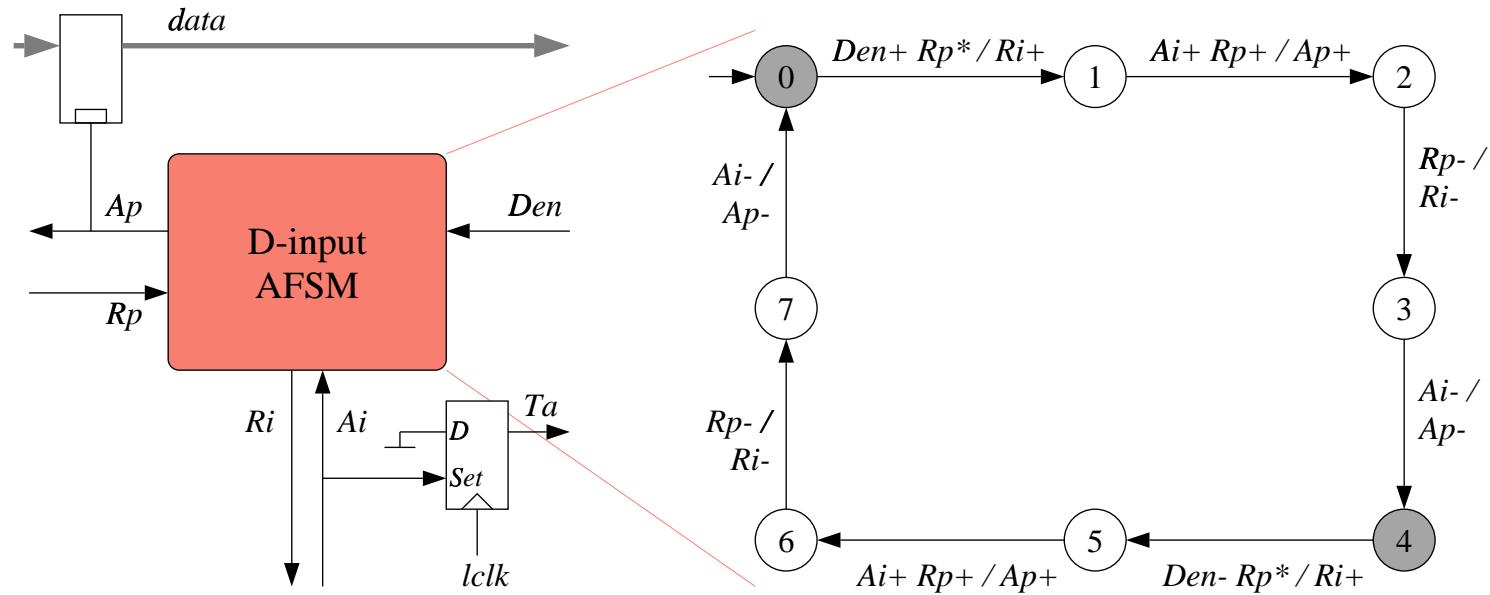

- Performs 2-phase to 4-phase conversion
- Transfer acknowledge ( $Ta$ ) indicates successful transfer
- 3D-tools available for synthesis (by K.Y. Yun)



## D-input port (cont.)


Synthesis results

$$R_i = R_p R_i + \overline{Den} Z_0 + Den \overline{A_p} \overline{Z_0}$$

$$A_p = R_p A_i + A_i A_p$$



$$Z_0 = \overline{R_p} Z_0 + \overline{A_i} Z_0 + Den \overline{R_p} A_p$$

2-level AND-OR  
Implementation

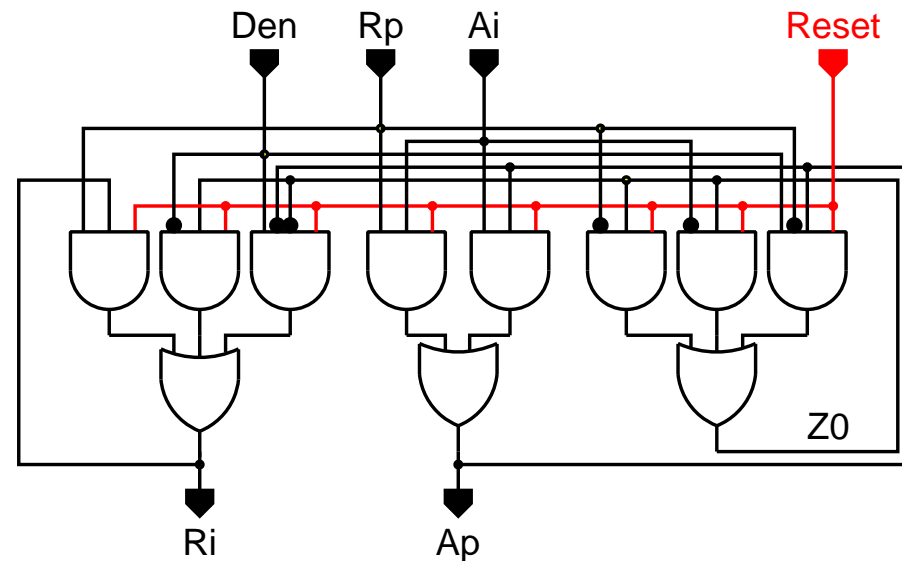


Compact, fast and hazard-free implementation of async FSM

# Data transfer mechanism

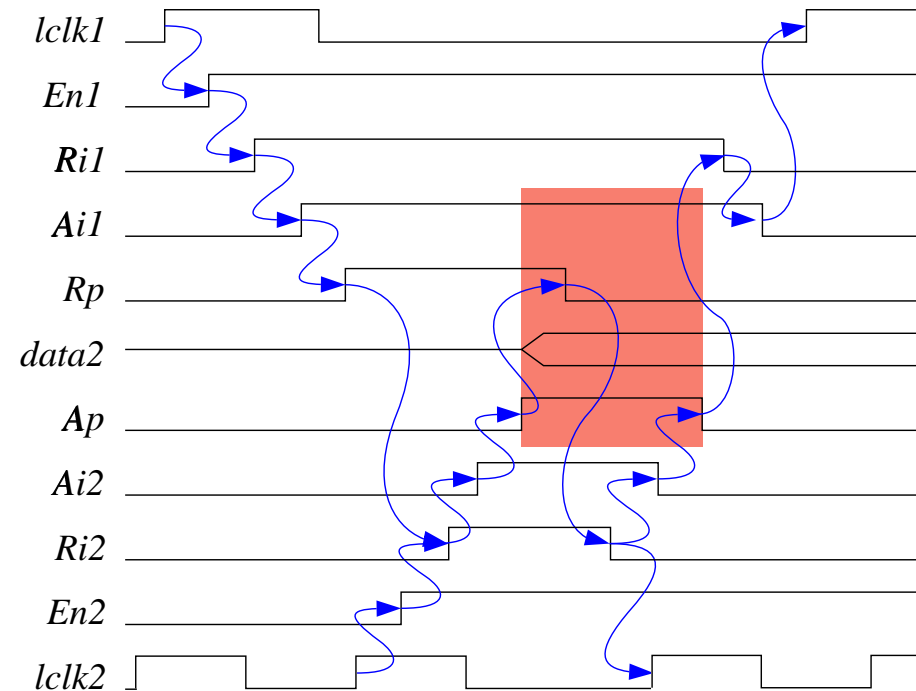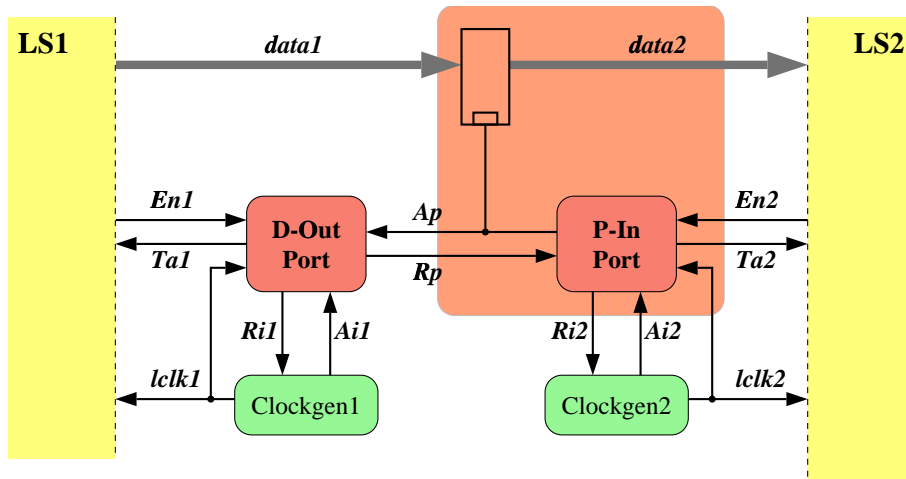

- The transfer channels all work with rendezvous scheme
- Push channels only, but pull channels would also be possible
- Data latches needed due to undetermined clock relation between the modules


# Data channel simulation

 

P-out to D-in  
channel:

- Clock stretching infrequent for P-ports
- Fast transfer processing
- Local clocks restart in phase with data


# SAFER cryptoalgorithm

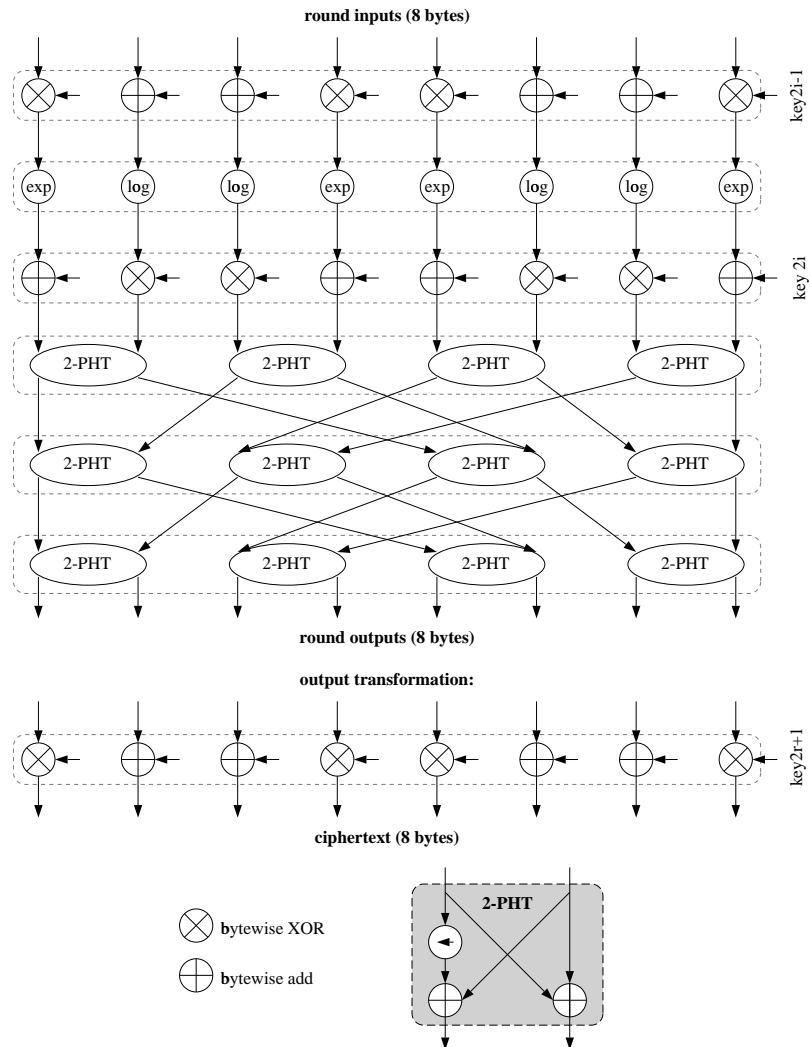


- Secret-key iterated block cipher
- Encryption and decryption slightly different
- Byte oriented: blocks of 8 bytes
- Recommended number of rounds 10 to 12
- Additional input/output transformation
- Comes with variable key lengths (Implemented version: SK-128)

# Cryptographic operation modes


## ECB Mode

 


## CFB mode

 

## CBC mode

 


## OFB mode

 

$p$  : Plaintext  
 $c$  : Ciphertext  
 $k$  : Key  
IV: Initialization Vector
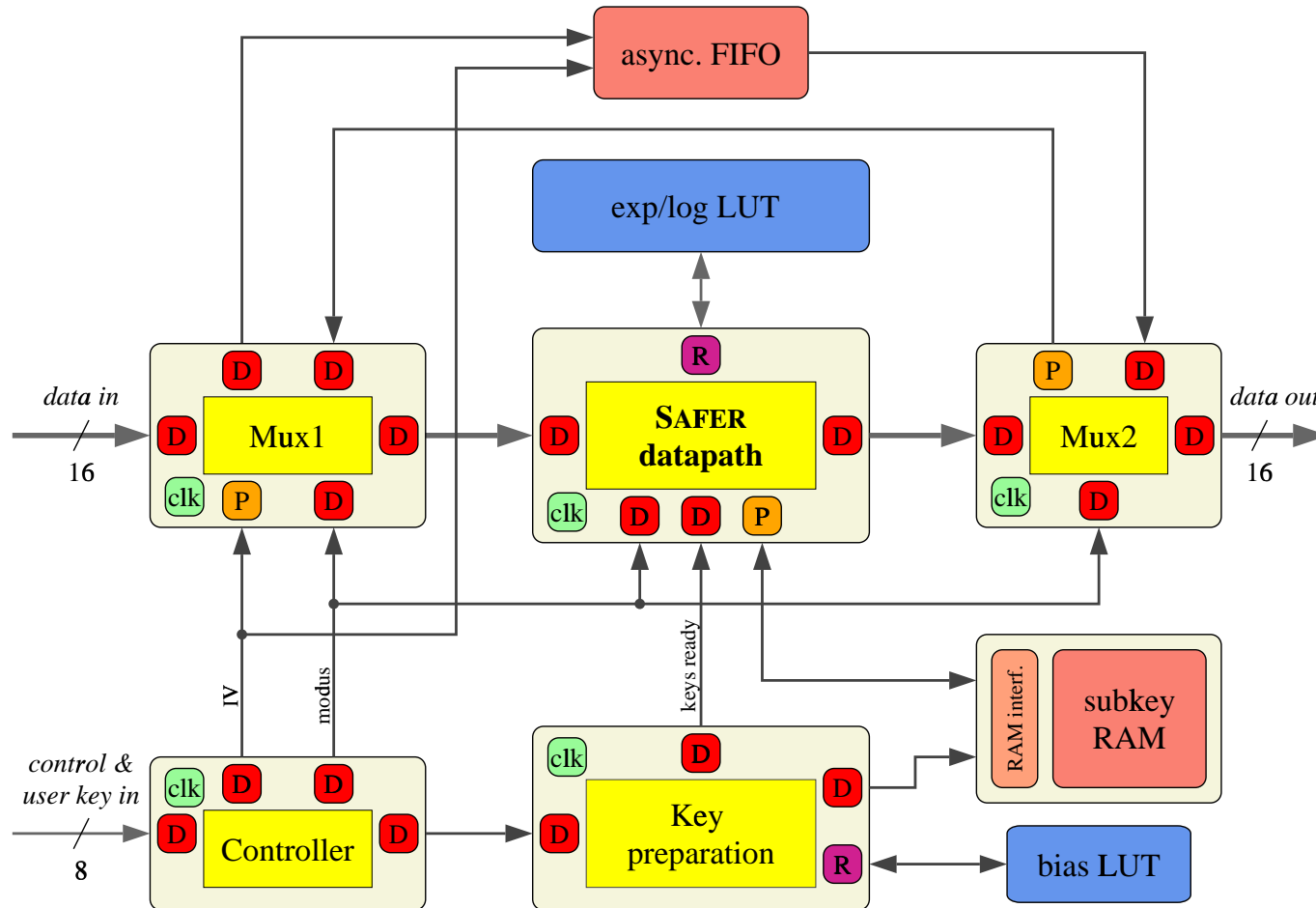
# Design Example: MARILYN SAFER cryptochip




- SAFER block cipher algorithm
- Supports ECB, CBC, CFB, OFB
- Implements both encryption and decryption
- 5 “true” clock domains
- Synchronous counterpart named “MERLIN”

# Area figures


	nominal cycle time	(sync.) module [ $\mu m^2$ ]	wrapper area w/o sync [ $\mu m^2$ ]	wrapper area with sync [ $\mu m^2$ ]
controller	2.1ns	38 457	12 501	18 315
key prep	3.4ns	250 299	13 059	18 531
bias ROM	1.2ns	32 805	4 104	4 104
datapath	3.3ns	214 956	28 629	37 863
mux1	2.3ns	150 831	29 628	39 204
mux2	2.2ns	126 747	26 361	34 227
exp/log ROM	1.7ns	291 672	12 708	12 708
subkey RAM	–	237 415	17 784	17 784
async FIFO	–	34 182	–	–
		1 377 364	144 774	182 736
		100%	10.5%	13.2%
	area			

# Design flow

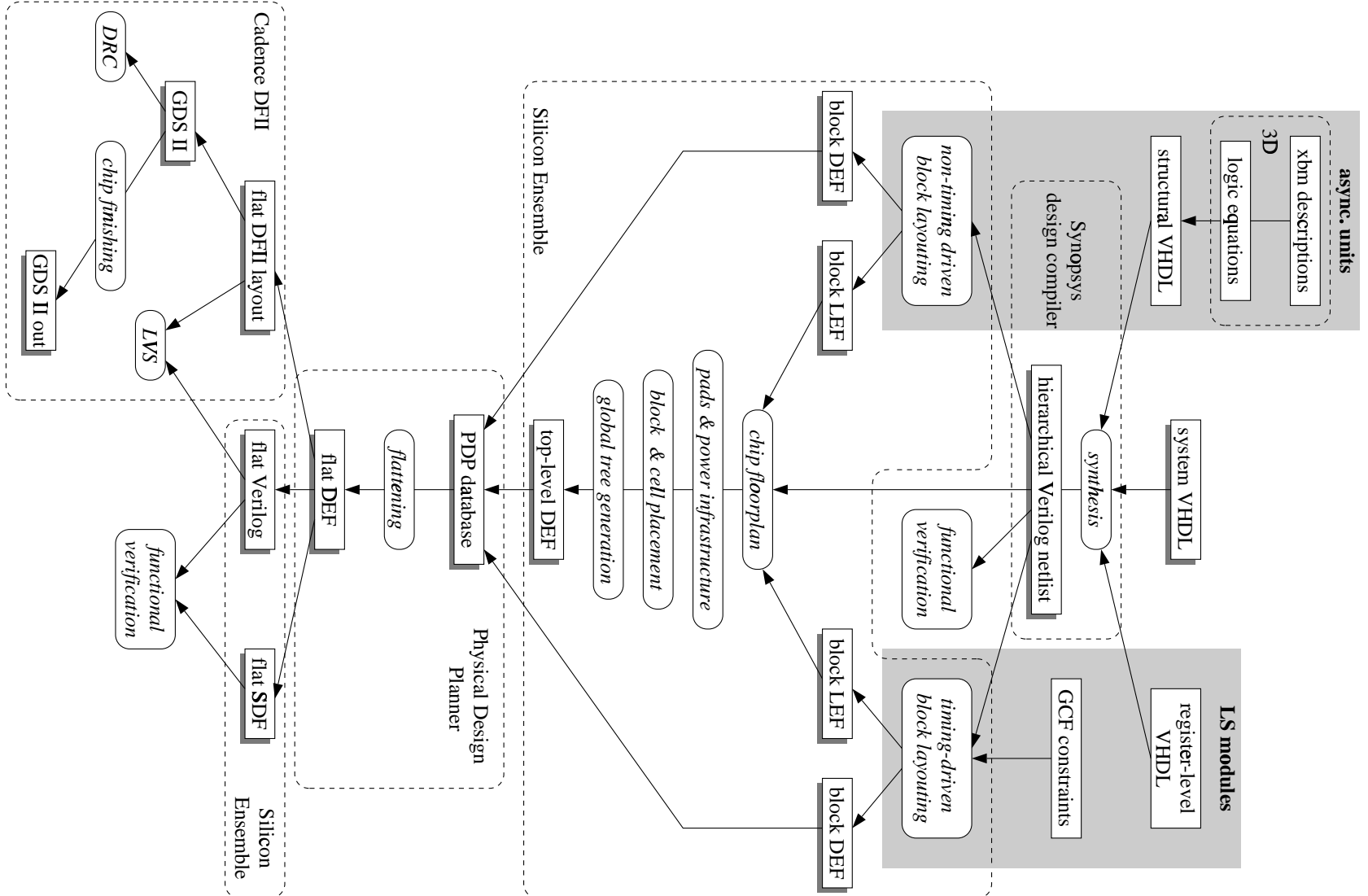



# MARILYN

 

- Technology:  
0.25 $\mu\text{m}$ , 5 metal, CMOS
- Core: 1.7 x 1.7 mm<sup>2</sup>
- Die: 2 x 2 mm<sup>2</sup>
- 66 pads ( $\rightarrow$  JLCC68 package)
- Contains extra testblocks for GALS components
- GALS overhead  $\approx$  10%
- Throughput 232Mbit/s at 10 rounds ECB
- Max. throughput up to 780Mbit/s (feedthrough)

# Results

			MARILYN (GALS)	MERLIN w/ clk-gating	MERLIN w/o clk-gating	GALS benefit
throughput	ECB enc.	10 rounds	232 MBit/s	303 MBit/s		-23%
		12 rounds	194 MBit/s	255 MBit/s		-24%
	CBC dec.	10 rounds	227 MBit/s	303 MBit/s		-25%
		12 rounds	191 MBit/s	255 MBit/s		-25%
energy / MBit	ECB enc. 10 rounds		555 nJ	737 nJ	973 nJ	25%
	CBC dec. 10 rounds		577 nJ	733 nJ	965 nJ	21%

# Conclusion

---

- Complete methodology for GALS architectures developed
- Over 25% energy reduction (energy per MBit throughput)
- Area overhead below 10%
- Throughput up to 25% lower than synchronous version (due to datapath not running at full speed, reason currently being investigated)
- GALS building blocks:
  - Consist mainly of technology independent structural VHDL
  - Only mutual exclusion (ME) element requires cell design
- And most important: GALS works on silicon!

# Future work

---

- Improve testability
- Extend the communication schemes beyond point to point links
- Address system level aspects like deadlock analysis and system partitioning
- Improve tool flow support (hierarchical flow, timing verification, integration of asynchronous tools)
- Possibility to withdraw a data transfer request (bus deferral)
- Power estimation theory
- Finer time-slice resolution of ring-oscillator