

VHDL Structural Modeling II

ECE-331, Digital Design

Prof. Hintz

Electrical and Computer Engineering

Ports and Their Usage


■ Port Modes

- **in** reads a signal
- **out** writes a signal
- **inout** reads or writes a signal
 - Can be connect to multiple signals
- **buffer** reads or writes a signal
 - Can be connected to only one signal
- **linkage** special use

Illegal Port Usage

- Signal Defined As “Out” Cannot Be Used As Signal Connected to Internal Device.
- Need to Create Internal Signal.
 
```
ENTITY (W, X,Y: IN bit ; A,B : OUT bit) ;
```



Constant-Valued Signals

- May Want to Hard-Wire an Input Signal to a Particular Value
 - Control signal in a model of real device, *e.g.*, preset or clear on a register
 - Inputs to MUX to implement a particular combinational logic circuit
 - Not use all inputs to a NAND/NOR gate while minimizing loading output of driving gate

Constant-Valued Signals

- Three Methods for Generating a Constant
 - Define local signal with default equal to desired value
 - *e.g.*, **signal** Zero_Input : **BIT** := '0' ;
 - Directly define input as '0' or '1' (VHDL-93)

Constant-Valued Signals

- Set default inputs on entity and use keyword **OPEN**

```
ENTITY NAND_2 IS  
  PORT ( A, B : IN BIT      := '1' ;  
          C   : OUT BIT      ) ;  
END NAND ;  
  
...  
X1 : NAND_2 ( OPEN, W, Z ) ;  
...  

```


Regular VHDL Structures

- Iterative Circuits Are Composed of Many Identical Circuits
 - Ripple-carry adder
 - RAM
 - Counters
 - Comparators

Generate Statement

- Use Generate Statement to Reduce Coding Effort
- Can Include Any Concurrent Statement Including Another Generate Statement
- Does Not Execute Directly, But Expands into Code Which Does Execute

Generate Statement

- Automatically Generates Multiple Component Instantiations
- Two Kinds of Statements
 - Iteration
 - **FOR . . . GENERATE**
 - Conditional
 - **IF . . . GENERATE**

Iteration

- Instantiates Identical Components
- **FOR** Syntax

```
identifier : FOR N IN 1 TO 8
```

```
GENERATE
```

```
concurrent-statements
```

```
END GENERATE name ;
```

- N is a constant and cannot be changed
- “name” is required

Conditional

- Takes Care of Boundary Conditions
- **IF** Syntax

```
identifier : IF (boolean expression)  
GENERATE  
  concurrent-statements  
END GENERATE name ;
```

- Cannot use “else” or “ifelse” clauses

Generate *e.g.*, R-C Adder

```
ENTITY RCAdder_16 IS  
PORT  
  ( A, B      : IN Bit_Vector (15 downto 0) ;  
    Cforce    : IN Bit ;  
    Sum       : OUT Bit_Vector(15 downto 0) ;  
    Cout      : OUT Bit ) ;  
END RCAdder_16 ;
```

Generate *e.g.*, R-C Adder

```
ARCHITECTURE Generate_S OF RCAdder_16 IS  
  COMPONENT Full_Addder  
  --defined elsewhere  
  PORT ( A, B, Cin : IN bit ;  
          S, Cout   : OUT bit );  
  END COMPONENT Full_Addder ;  
  
  SIGNAL Int_C : BIT_VECTOR (15 DOWNTO 0) ;
```

Generate *e.g.*, R-C Adder

```
BEGIN    --RC Adder
All_Bits:
FOR I IN 15 DOWNTO 0 GENERATE
LSB :
IF ( I = 0 ) GENERATE
BEGIN
S0: Full_Adder
PORT MAP ( A(I), B(I), Cforce,
            Sum(I), Int_C(I) );
END GENERATE S0 ;
```


Generate *e.g.*, R-C Adder

```
Middle_bits:
```

```
IF ( I < 15 AND I > 0 ) GENERATE
```

```
BEGIN
```

```
SI: Full_Adder
```

```
PORT MAP ( A(I), B(I), Int_C(I-1),  
            Sum(I), Int_C(I) );
```

```
END GENERATE SI;
```

Generate *e.g.*, R-C Adder

MSB :

```
IF ( I = 15 ) GENERATE
```

```
BEGIN
```

```
S15: Full_Adder
```

```
PORT MAP ( A(I), B(I), Int_C(I-1),  
            Sum(I), Cout );
```

```
END GENERATE MSB;
```

```
END GENERATE All_Bits
```

```
END Generate_S ;
```

Unconstrained Ports

- Entity Declarations Can Have Ports Defined Using Arrays Without Explicitly Including the Size of the Array
- Leads to General Specification of Iterative Circuit
- Uses Predefined Array Attribute **'LENGTH**

Generate *e.g.*, R-C Adder

```
ENTITY RCAdder_N IS  
PORT ( A, B      : IN  Bit_Vector ;  
        Cforce    : IN  Bit   ;  
        Sum       : OUT Bit_Vector ;  
        Cout      : OUT Bit   ) ;  
END RCAdder_N ;
```

Generate *e.g.*, R-C Adder

```
ARCHITECTURE Generate_S OF RCAdder_N IS  
  COMPONENT Full_Adder --defined elsewhere  
    PORT ( A, B, Cin : IN bit ;  
           S, Cout   : OUT bit ) ;  
  END COMPONENT Full_Adder ;  
  
SIGNAL Int_C : BIT_VECTOR  
          ( (A'LENGTH - 1) DOWNTO 0 ) ;
```

Generate *e.g.*, R-C Adder

```
BEGIN --RC Adder
All_Bits:
FOR I IN (A'LENGTH -1) DOWNTO 0 GENERATE
LSB:
IF (I = 0) GENERATE
BEGIN
S0: Full_Addder
PORT MAP ( A(I), B(I), Cforce,
           Sum(I), Int_C(I) );
END GENERATE S0 ;
```


Generate *e.g.*, R-C Adder

Middle_bits :

```
IF ( I < ( A'LENGTH - 1 ) AND I > 0 )
```

```
GENERATE
```

```
BEGIN
```

```
SI: Full_Adder
```

```
PORT MAP ( A(I), B(I), C(I-1),
```

```
Sum(I), Int_C(I) );
```

```
END GENERATE SI ;
```

Generate *e.g.*, R-C Adder

MSB:

```
IF ( I = A'LENGTH - 1 ) GENERATE  
BEGIN
```

```
    SN: Full_Adder
```

```
        PORT MAP ( A(I), B(I), INT_C(I-1),  
                    Sum(I), Cout );
```

```
    END GENERATE MSB;
```

```
END GENERATE All_Bits
```

```
END Generate_S ;
```

Arithmetic Operators

■ Four Classes of Operators in VHDL

- Logic
- Relational
- Shift
- Arithmetic

+ **-** ***** **/** ******
mod **rem** **abs** **&** (concatenation)

Number Types

■ Integer Literals

MAX_INT = Maximum Positive Value of Integer

Positive Numbers = $\{ 1, 2, 3, \dots, \text{MAX_INT} \}$

Counting Numbers = $\{ \text{Positive Numbers} \} \cup \{ 0 \}$

Integers = \pm Counting Numbers

Number Types

■ Floating Point Literals

- Number containing a radix point
- Only one type, REAL
- Range of values is implementation dependent

Type Conversion

- There is NO implicit type conversion
 - Mixed type operations are not allowed
- Explicit type conversion IS allowed
 - *e.g.*, **INTEGER** (4.8), **REAL** (5)

Arithmetic Operator Limitations

- **REM** and **MOD** Operators Only Defined for Integers
- ****** (Exponentiation) Accepts Both Integer and Real Arguments With Restrictions
 - **REAL** can only be raised to integer power
 - **INTEGER** can only be raised to positive power


Writing Literals

- Underscore Can Be Inserted Anywhere for Readability
- Exponential Notation Allowed for Both Integers and Reals
- Any Radix From 2 to 16 Is Allowed
 - radix # number_in_radix #

Literal Examples

- Decimal Integer, *e.g.*,
 - 43800, 43_800, 438e2, 438E+2
- Other Radix Integer, *e.g.*,
 - 2#1101011#, 3#21201#, 16#faff0#
- Real, *e.g.*,
 - 0.0, 0.0_26, 3.8e-4, 9.8E+4
- Other Radix Real, *e.g.*,
 - 2#11.011#, 3#22.1#, 7#46.31#e-1

End of Lecture

 

- Ports
- Constants
- Regular Structures
- Arithmetic Operators
- Literals