

Example of Scheduling and Allocation




Version 2, September 2000

Jaap Hofstede


```
#define m1 ...
#define m2 ...
#define m3 ...
#define m4 ...

main()
{ float t, i1, o1, d1=0.0, d2=0.0;
  while (1) {
    in(i1);
    t = i1 + m3*d2 + m1*d1;
    o1 = t + m4*d2 + m2*d1;
    d2 = d1; d1 = t;
    out(o1);
  }
}
```


Specification in C

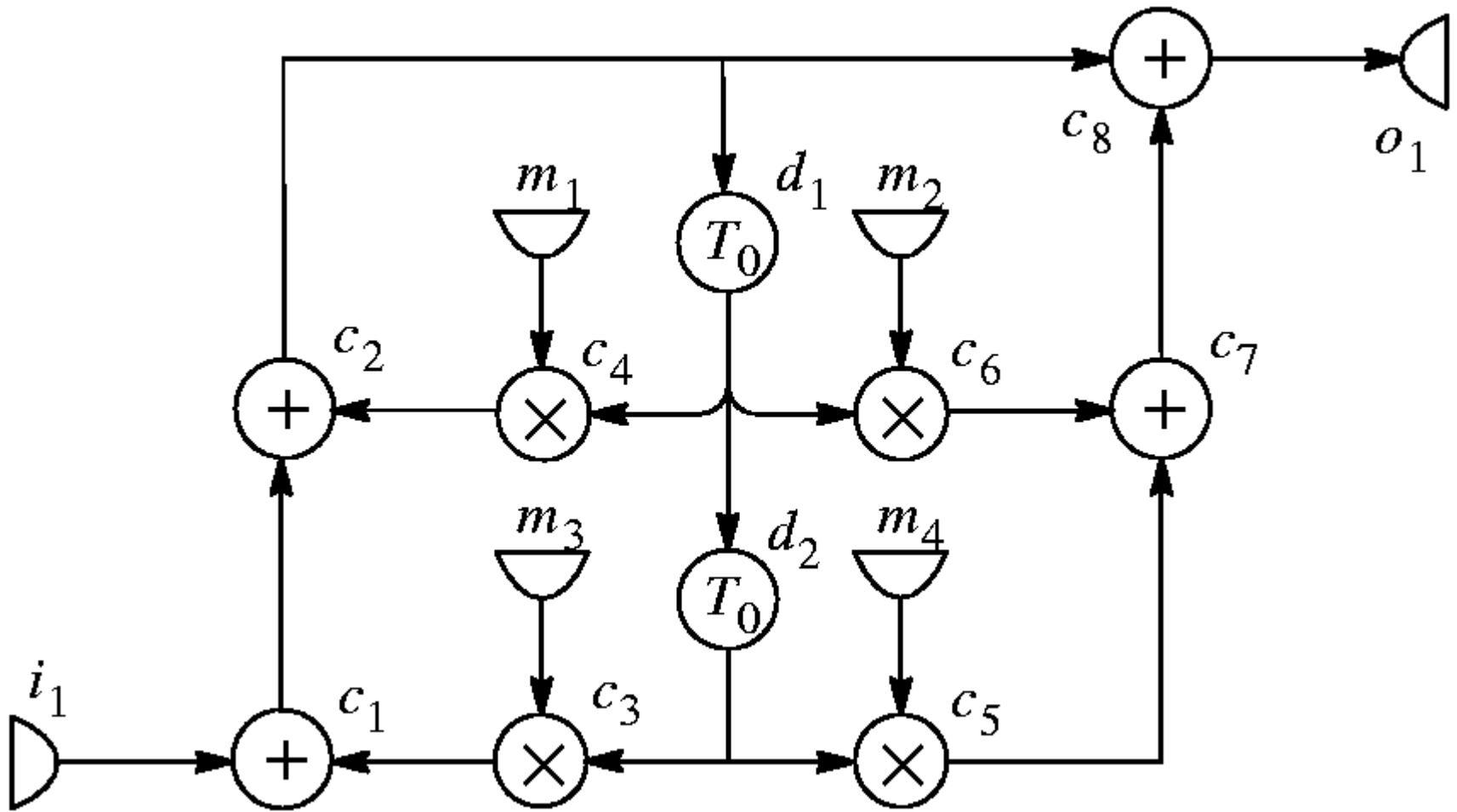


Original dataflow graph

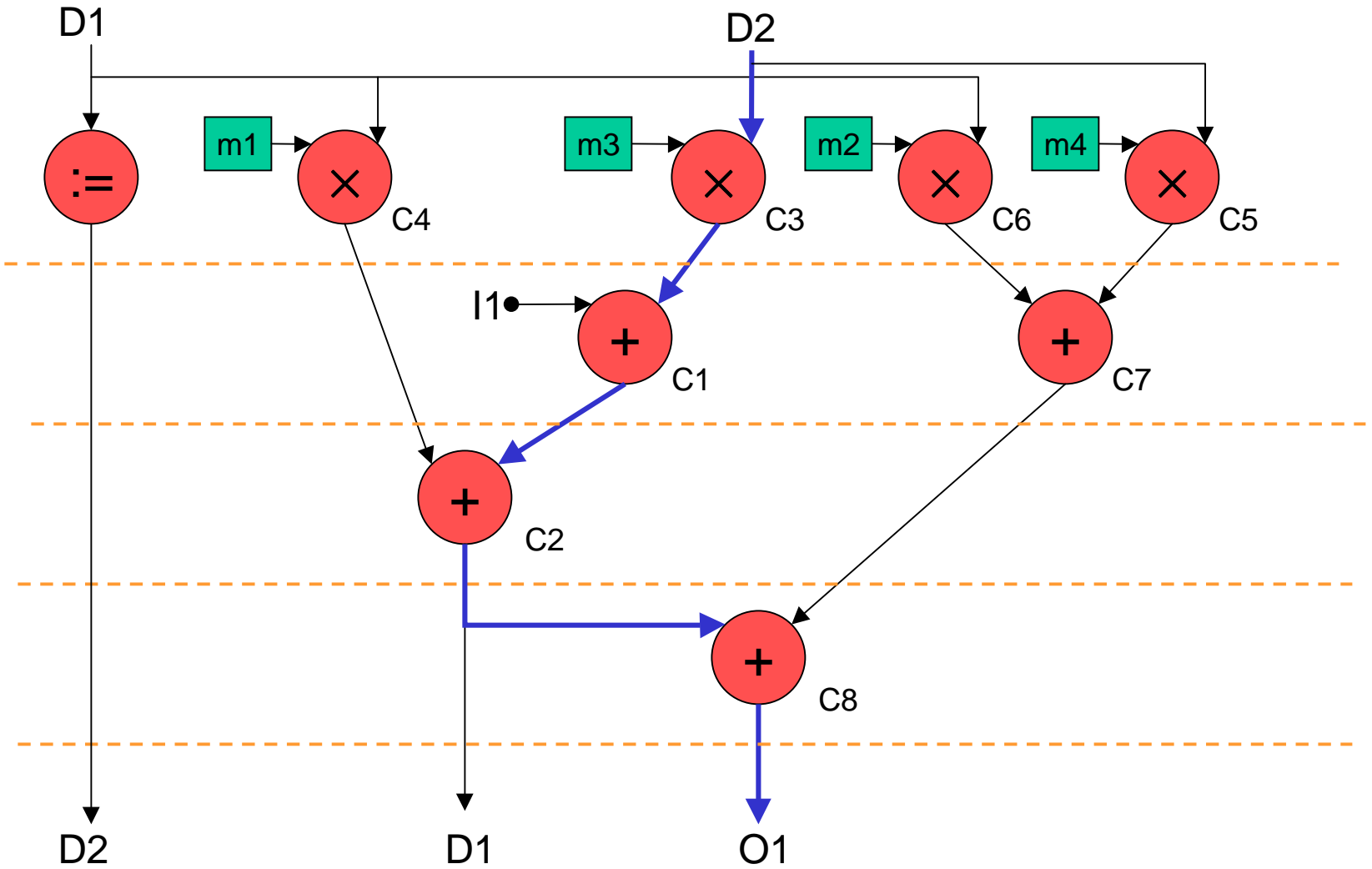


ASAP (4)

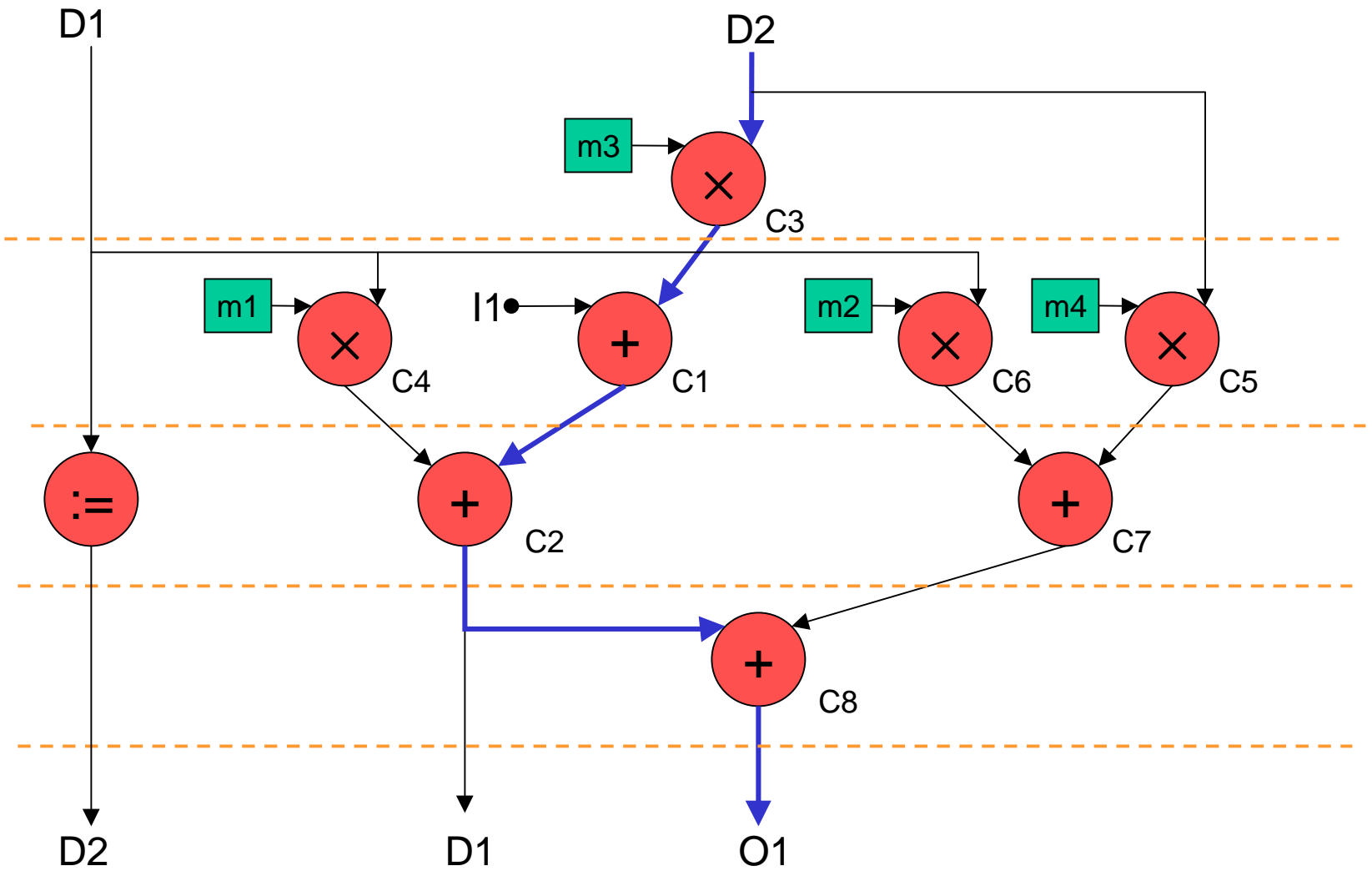



ALAP (4)

 


1 Adder, 1 multiplier (6)

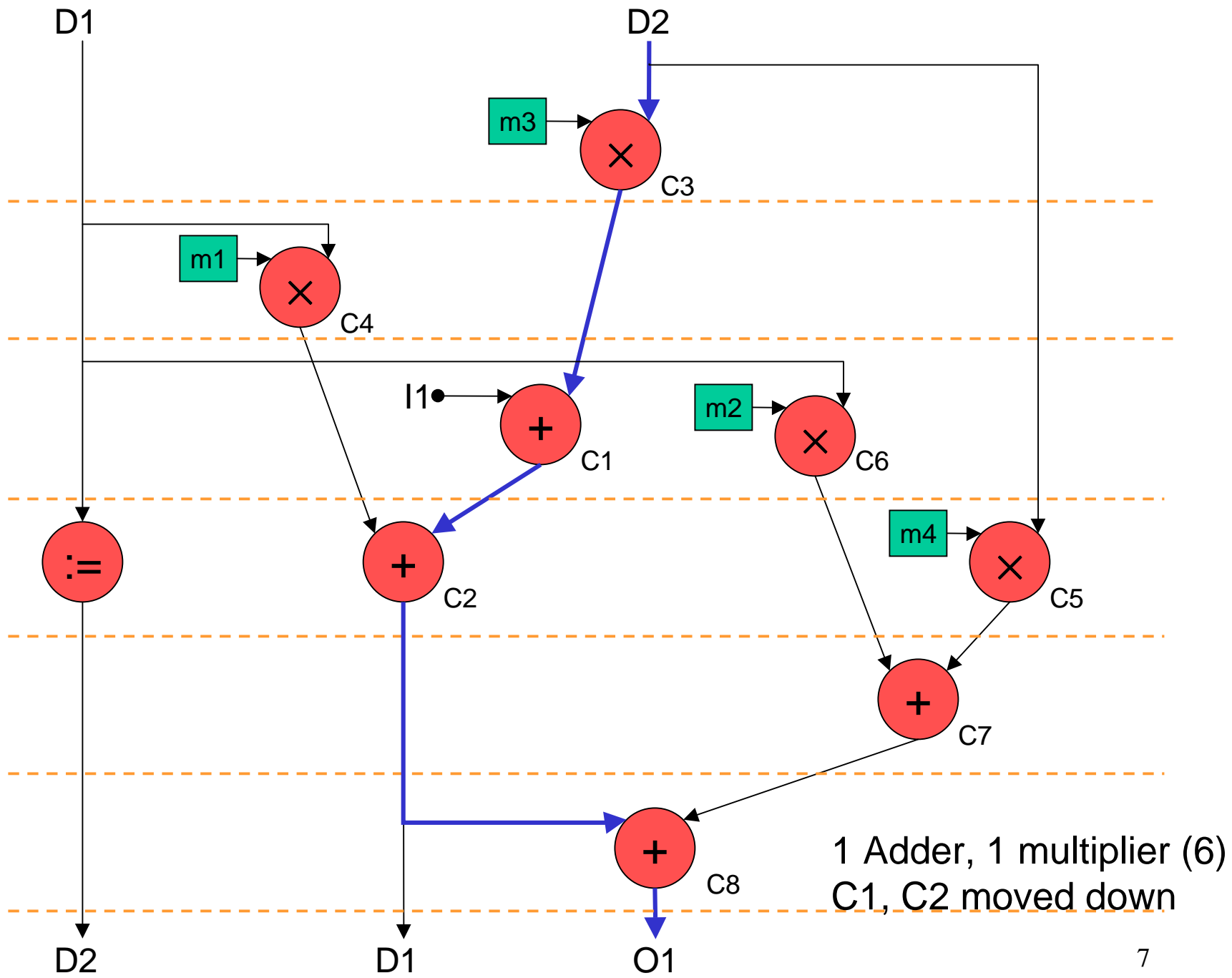


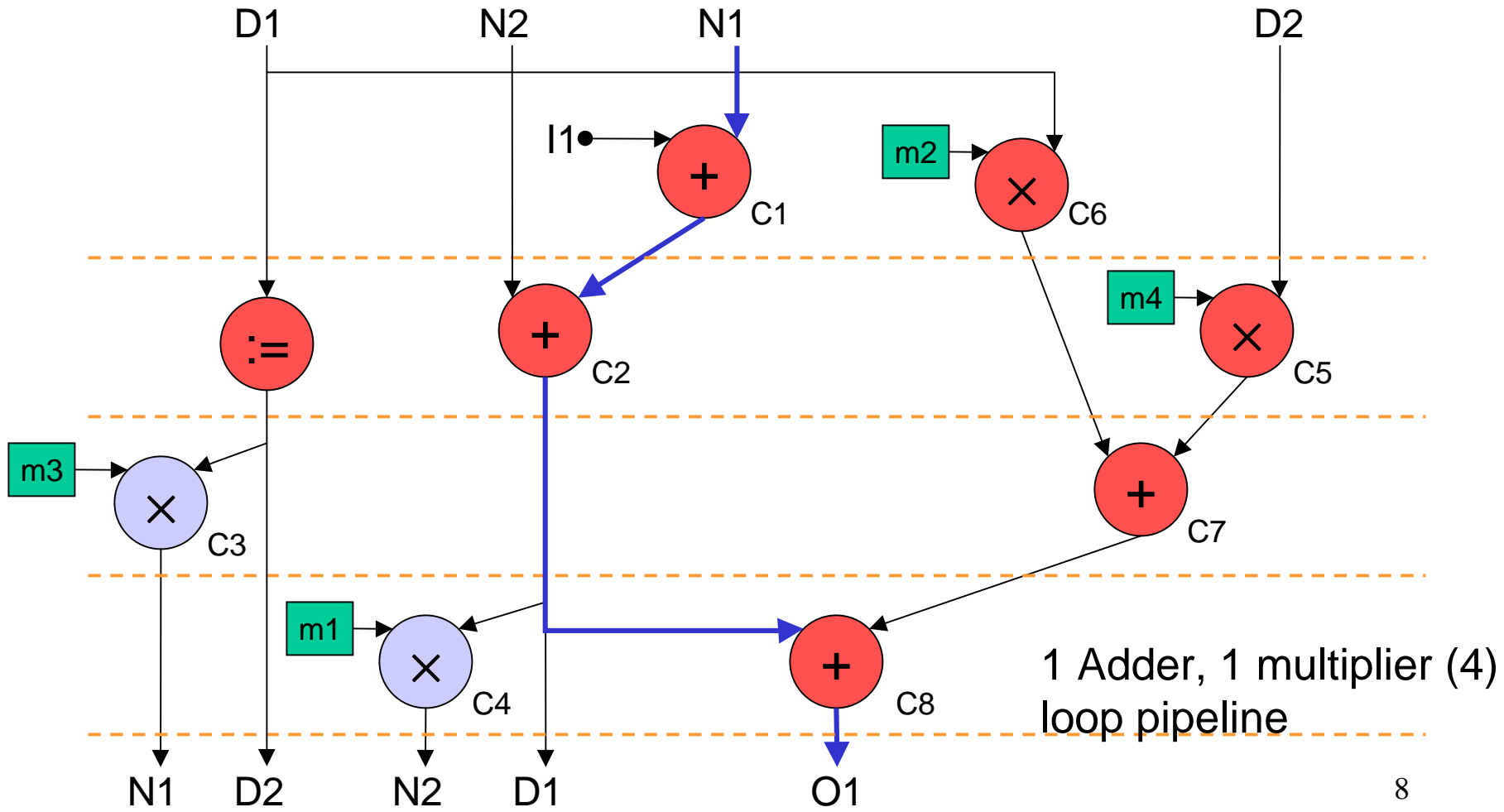

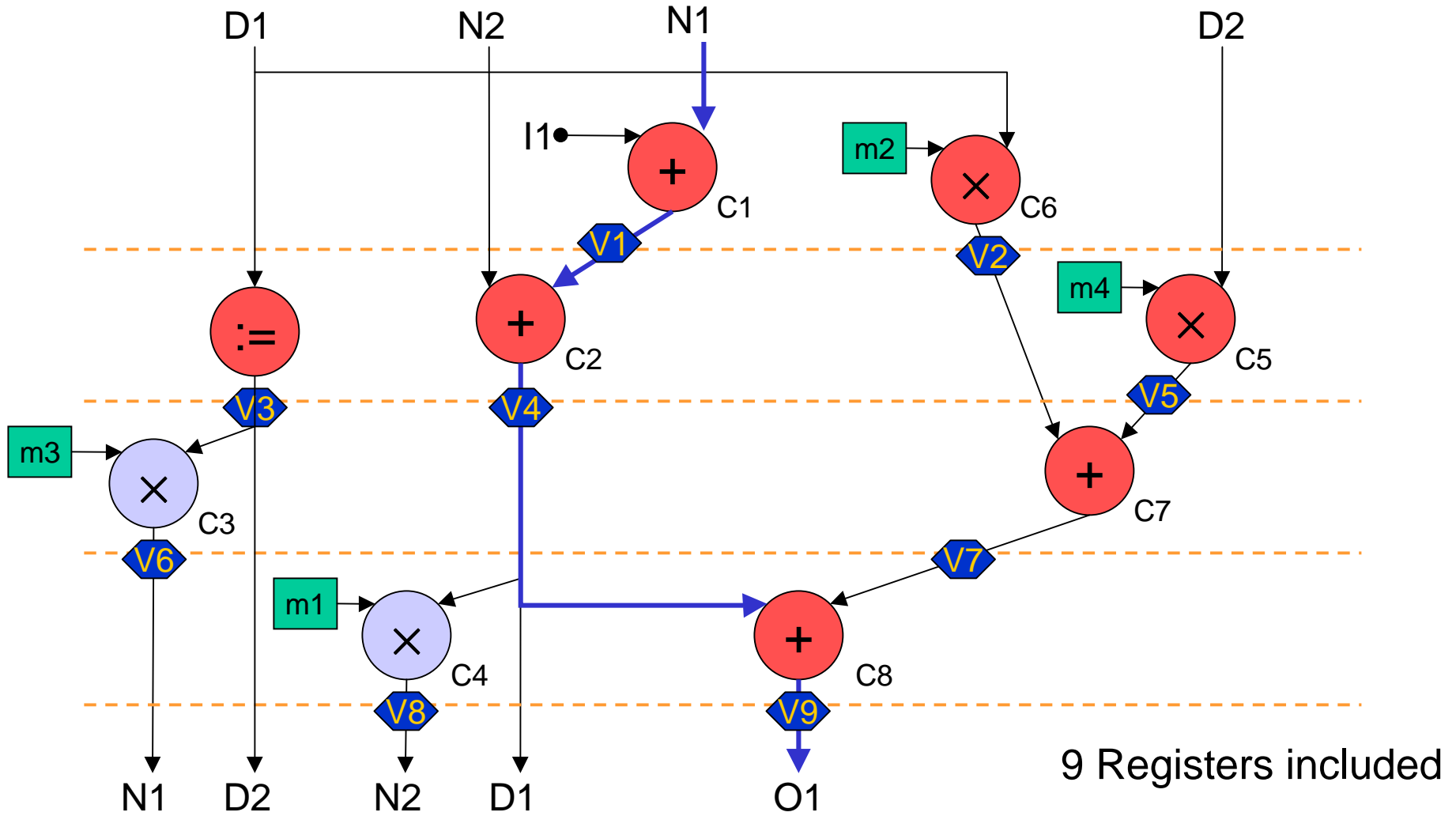


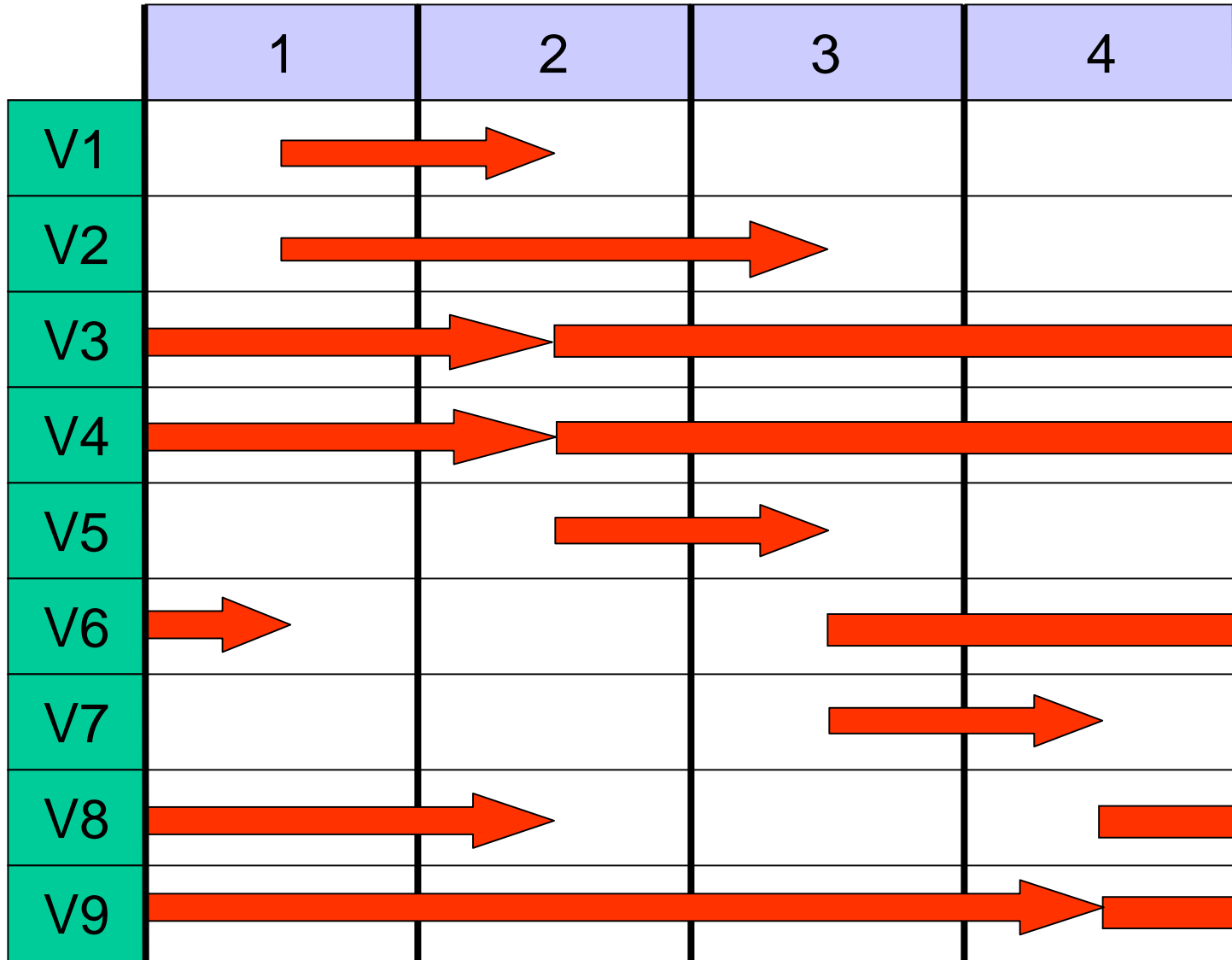


Lifetimes of registers

 

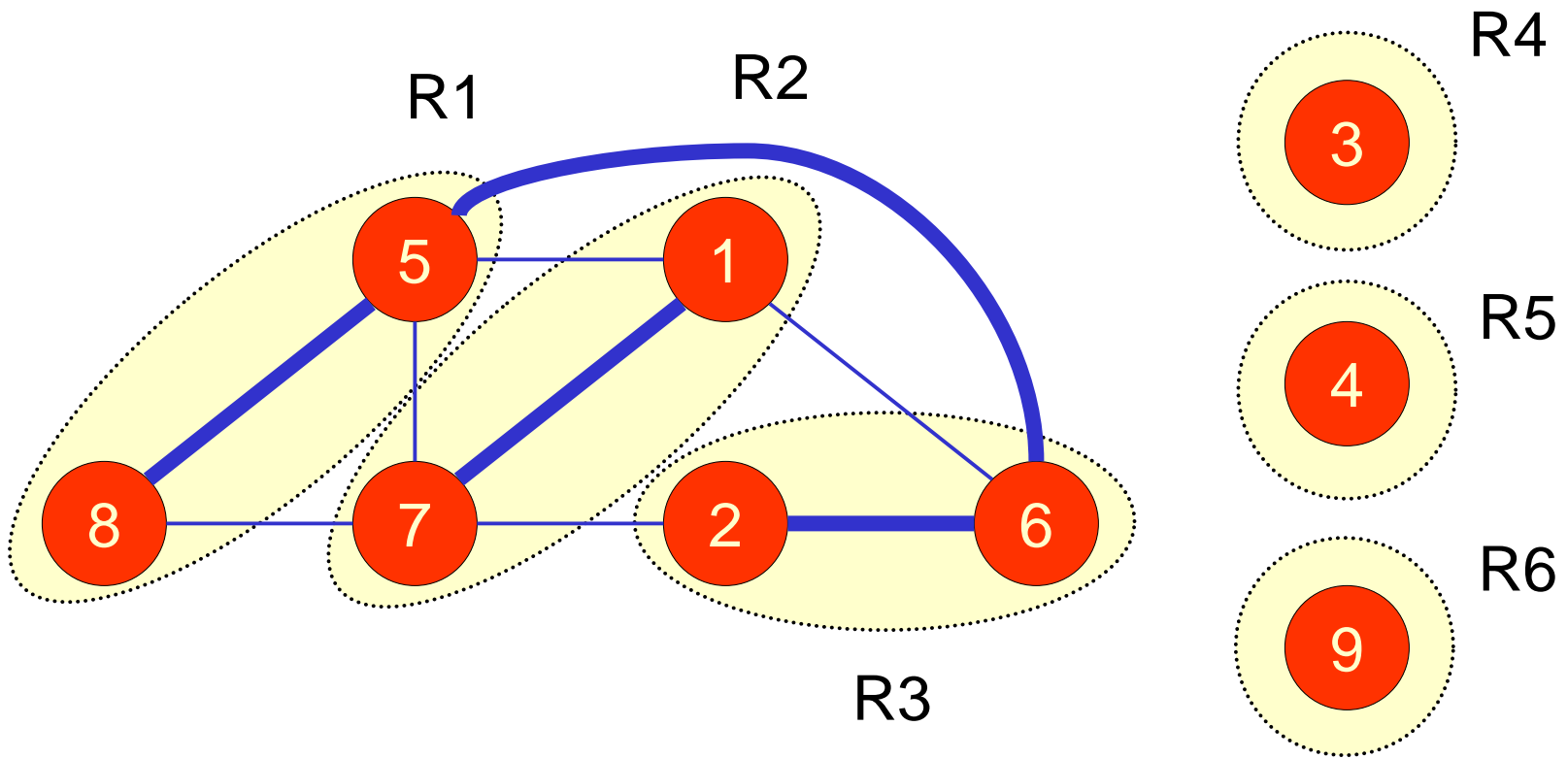Lifetime compatibility graph
 (+ x := is source of data)




Clique partitioning

 


Numbers are time steps

Corresponding non-optimised data path

Numbers are time steps

 

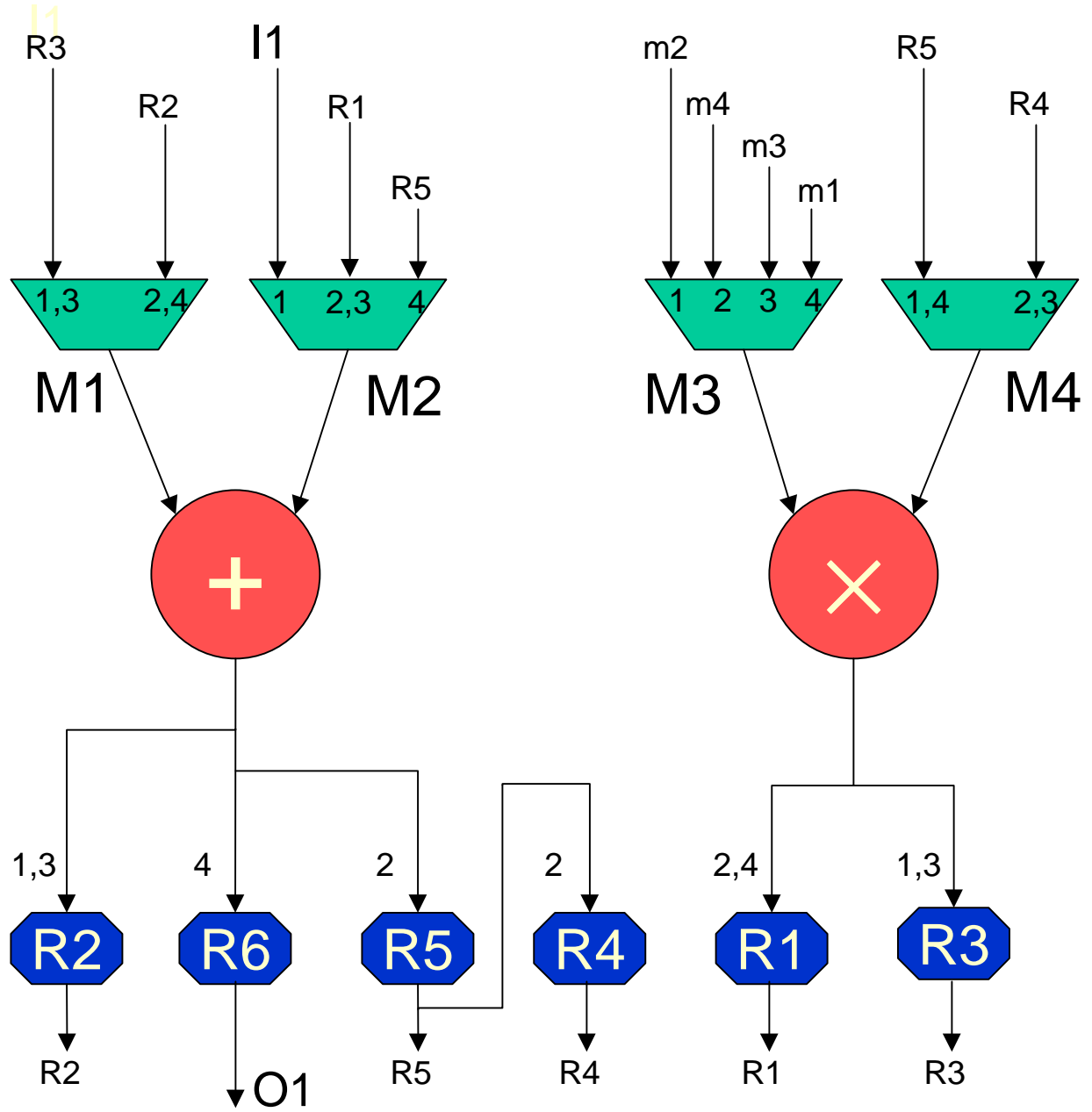Multiplexers
optimised by
commutative
property



Size of multiplexers reduced

Controller-1

- All six registers have an enable input, *ena*
Rx.ena
- M1 and M4 have 1 control input, *s*:
Mx.s
- M2 and M3 have 2 control inputs, *s1* and *s0*:
Mx.s1 and **Mx.s0**
- Controller has four states:
State1, State2, State3, State4

Controller-2

State	enable						M1	M2		M3		M4
	R1	R2	R3	R4	R5	R6	s	s1	s0	s1	s0	s
1	0	1	1	0	0	0	0	0	0	0	0	0
2	1	0	0	1	1	0	1	0	1	0	1	1
3	0	1	1	0	0	0	0	0	1	1	0	1
4	1	0	0	0	0	1	1	1	0	1	1	0

$R1.ena = M1.s = M3.s0 = State2 + State4$

$R2.ena = R3.ena = State1 + State3$

$R4.ena = R5.ena = State2$

$R6.ena = M2.s1 = State4$

$M2.s0 = M4.s = State2 + State3$

$M3.s1 = State3 + State4$