
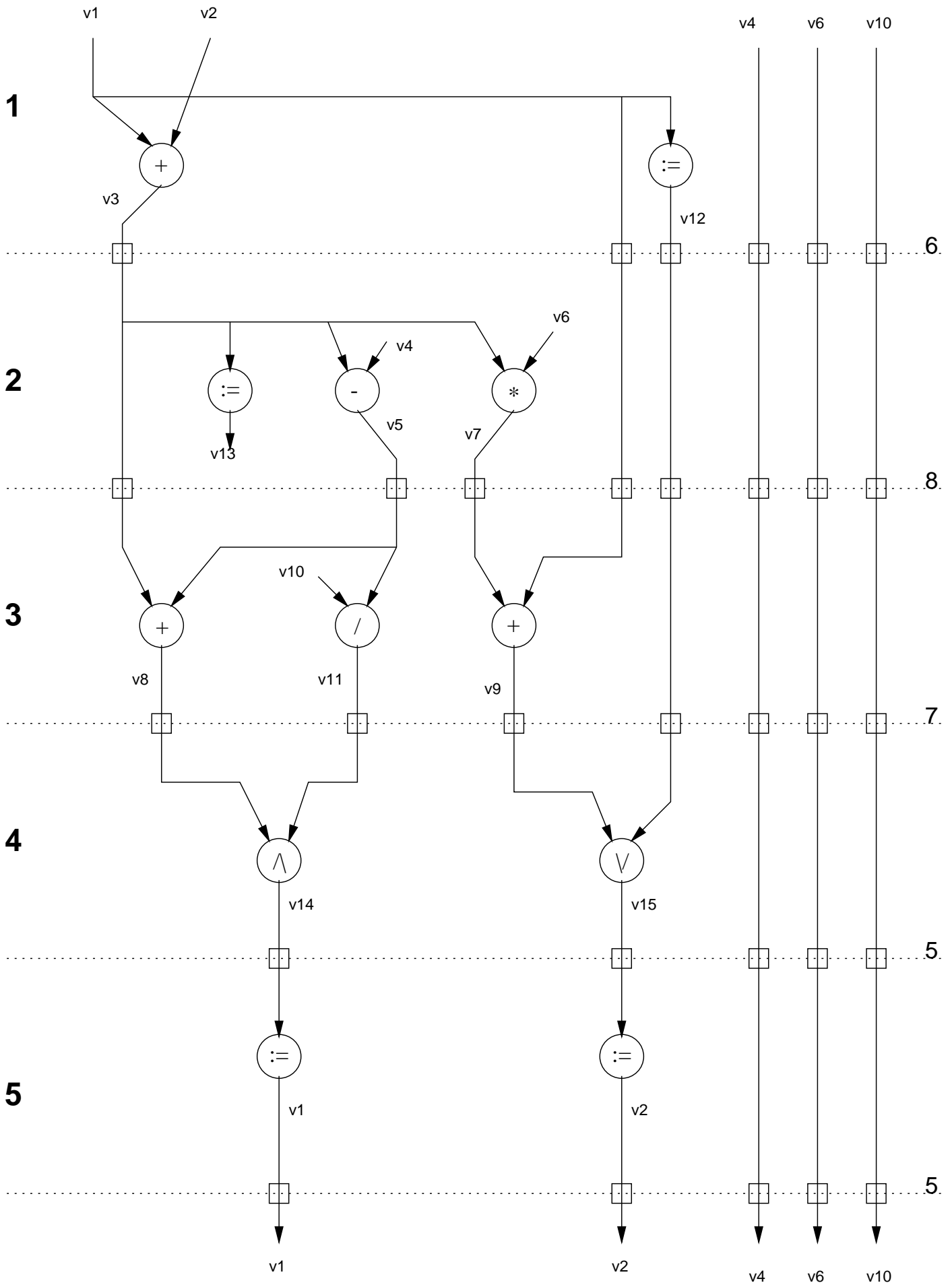



Allocation 1: Original scheduled data-flow graph

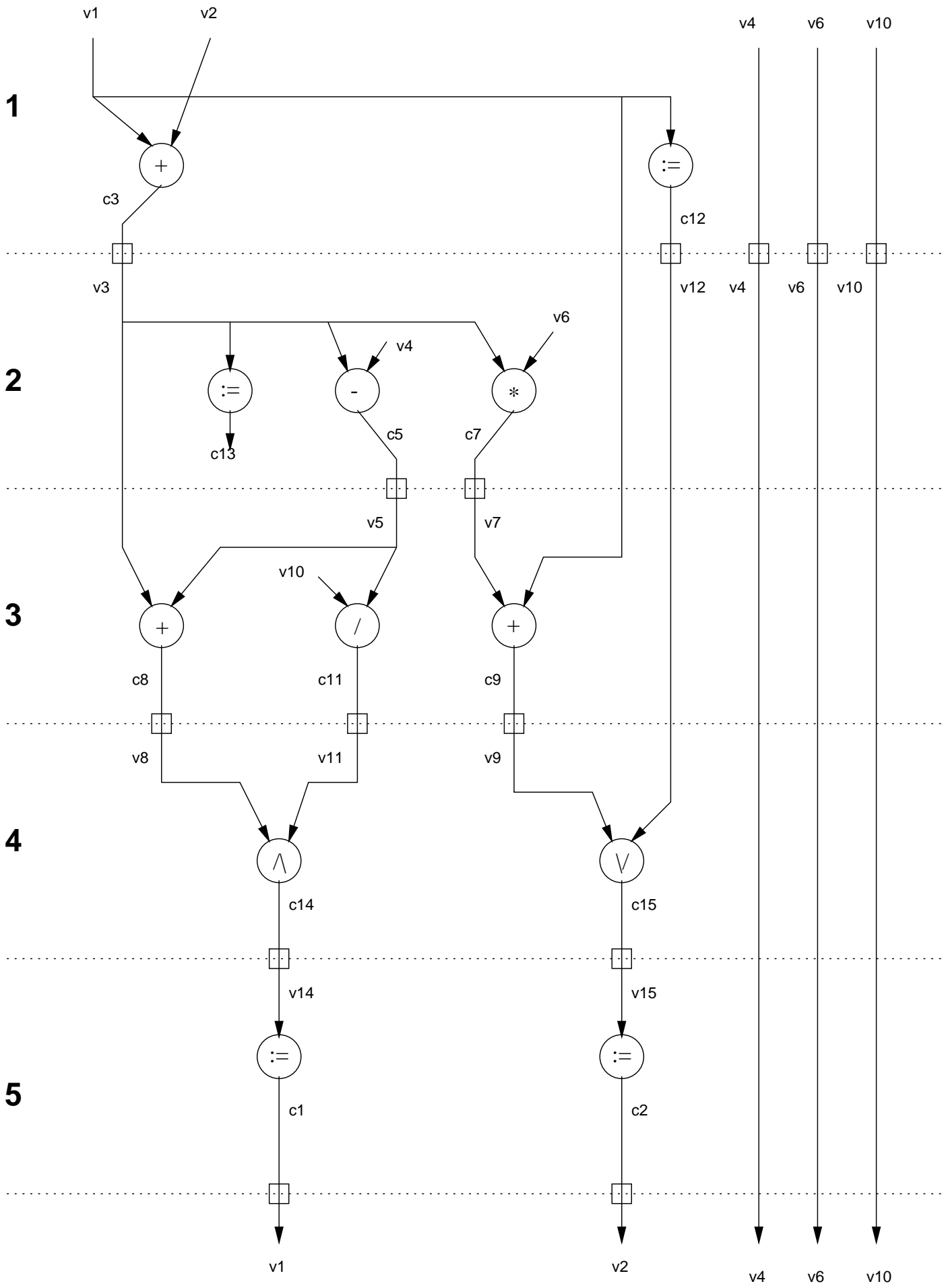



Allocation 2: Registers inserted





Allocation 3: Reduced number of registers

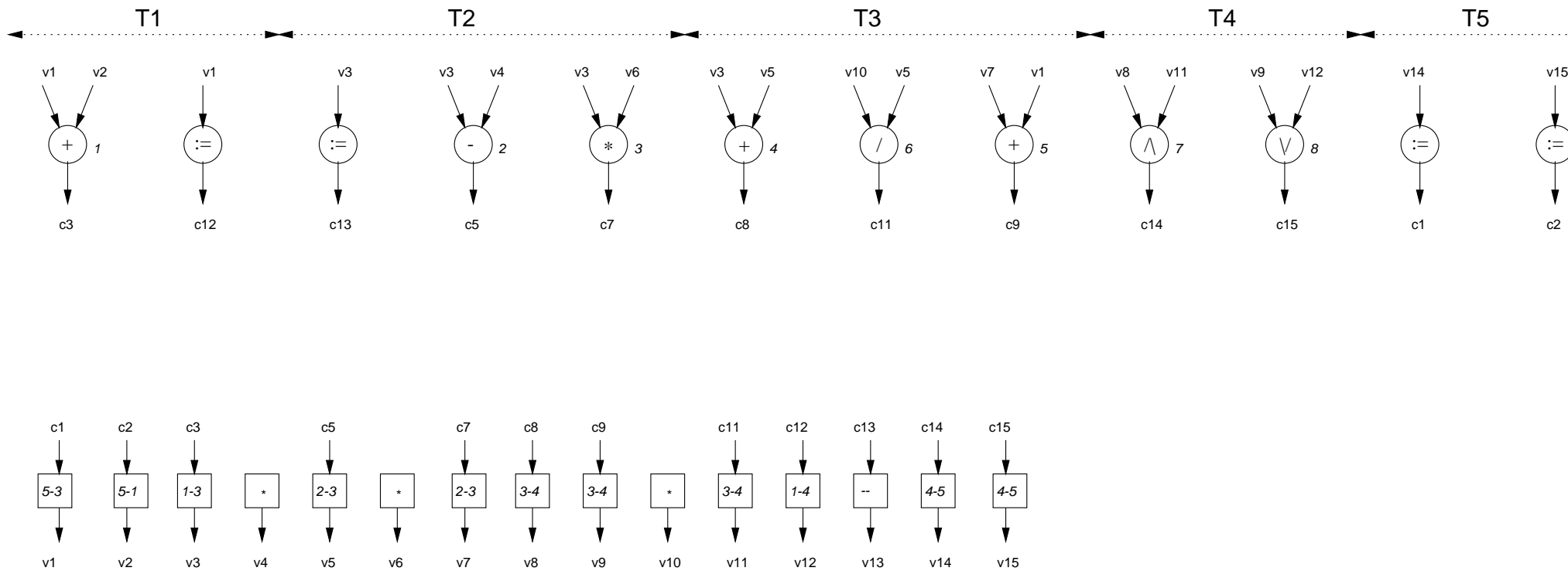


Allocation 4: Same picture as 3, but different layout

 
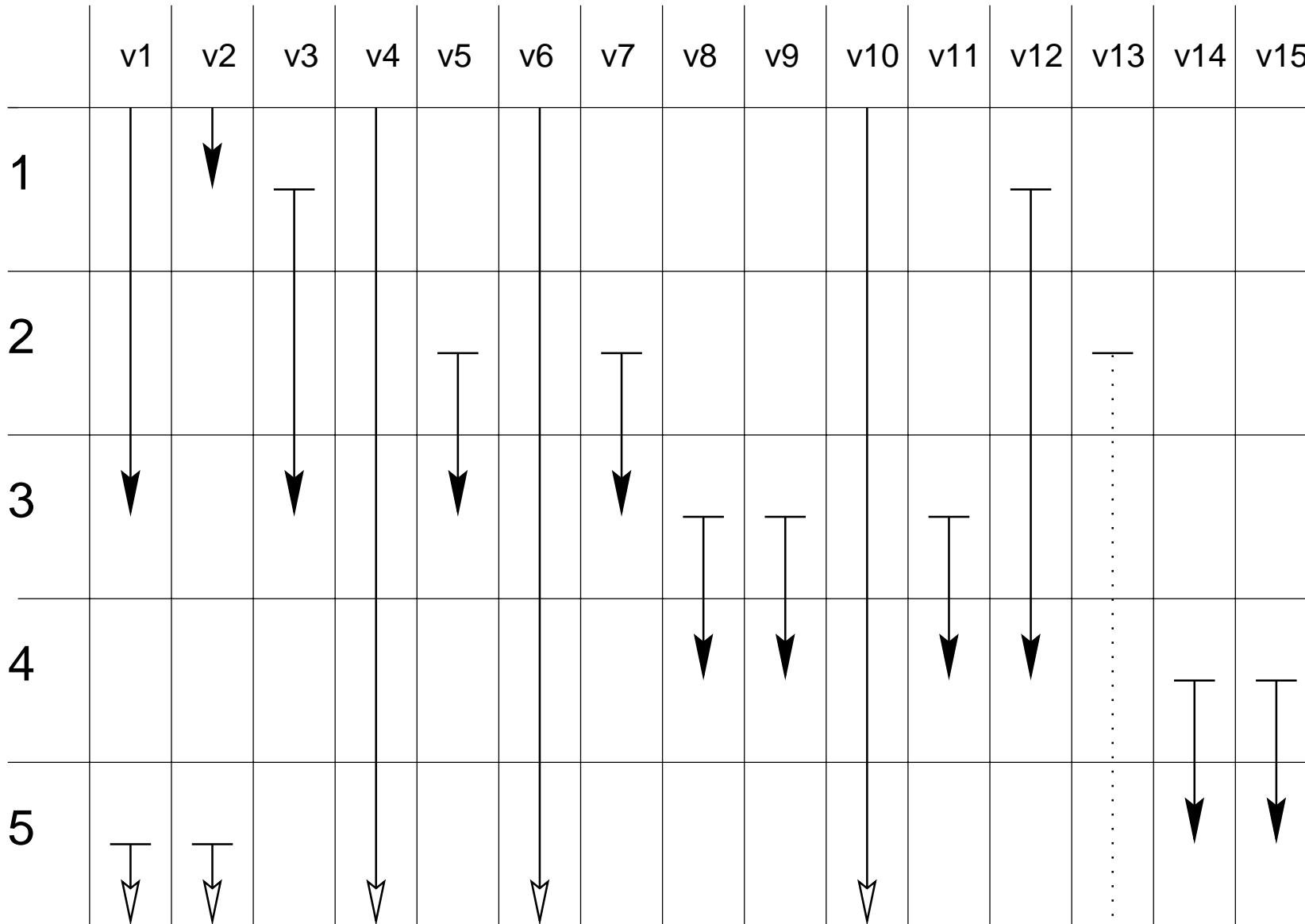


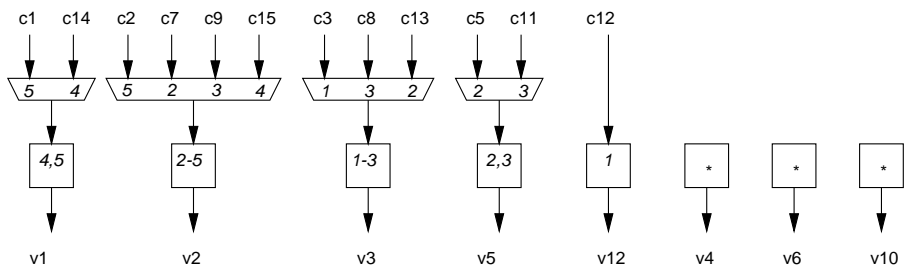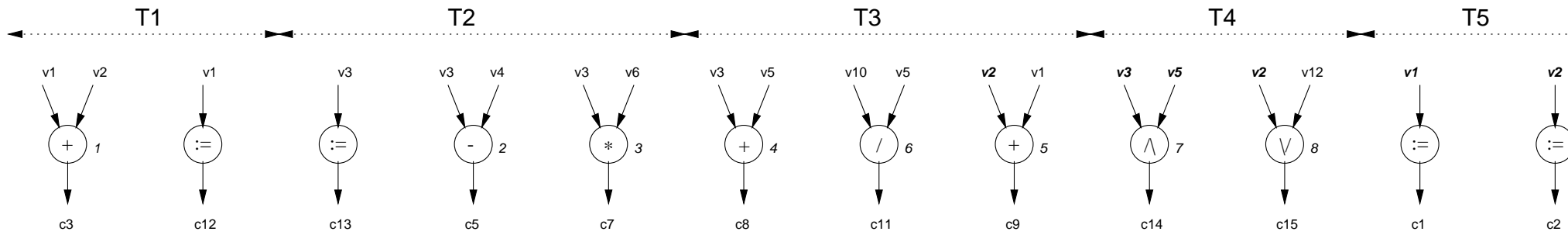



Allocation 5: Registers optimized

 


Allocation 6: State 5 deleted; v13 deleted

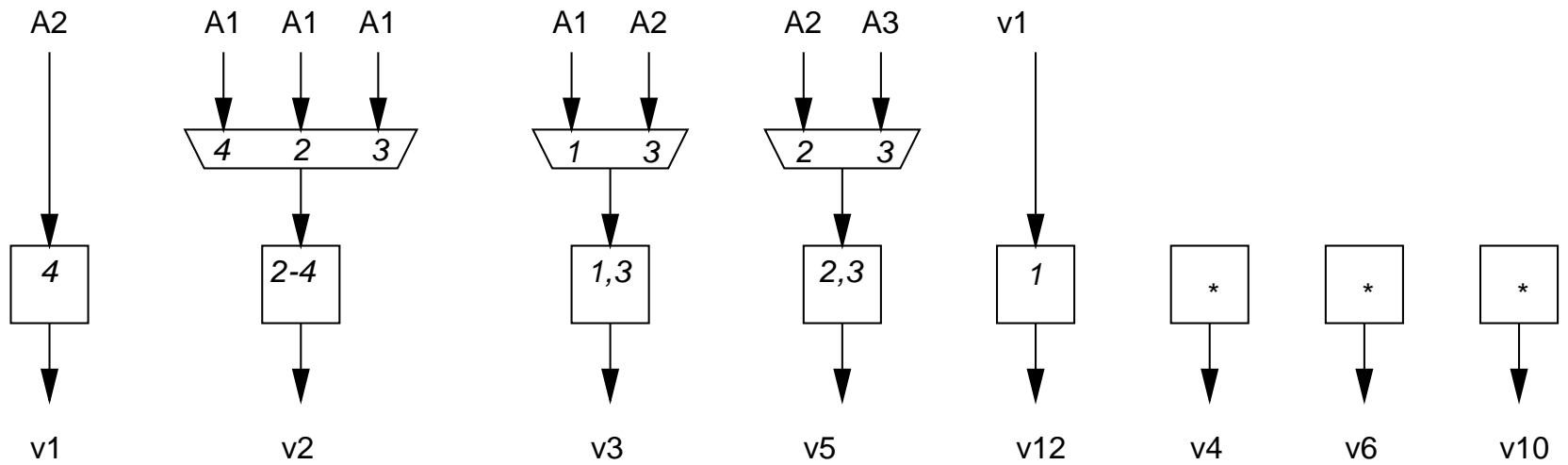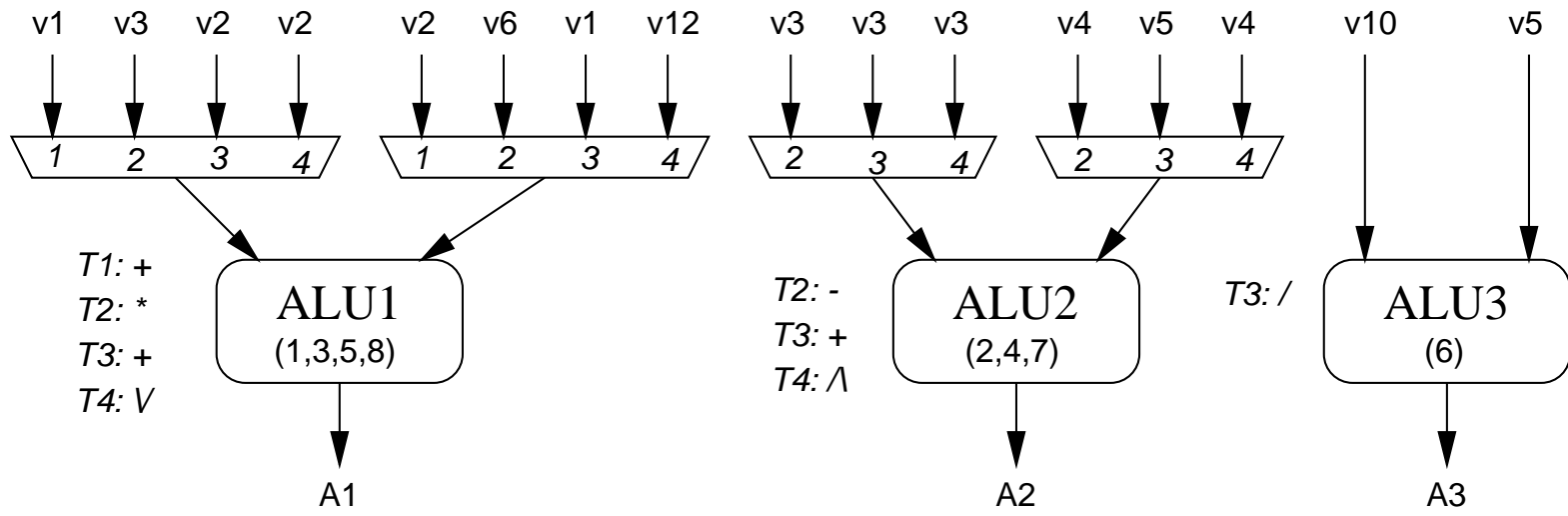

Allocation 7: Operations allocated to ALU's

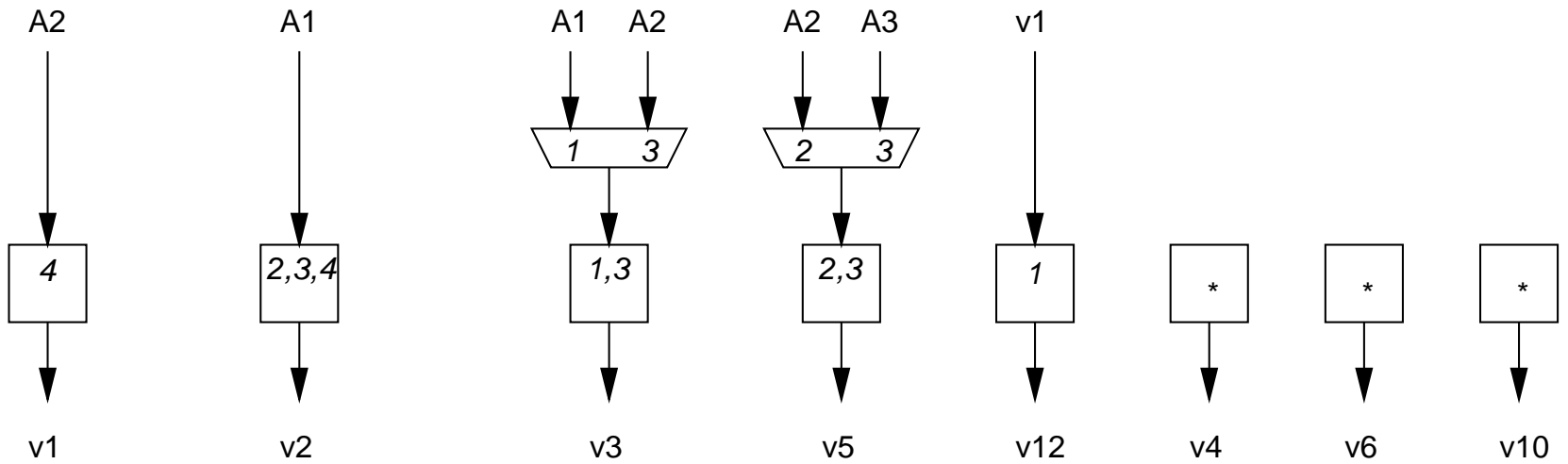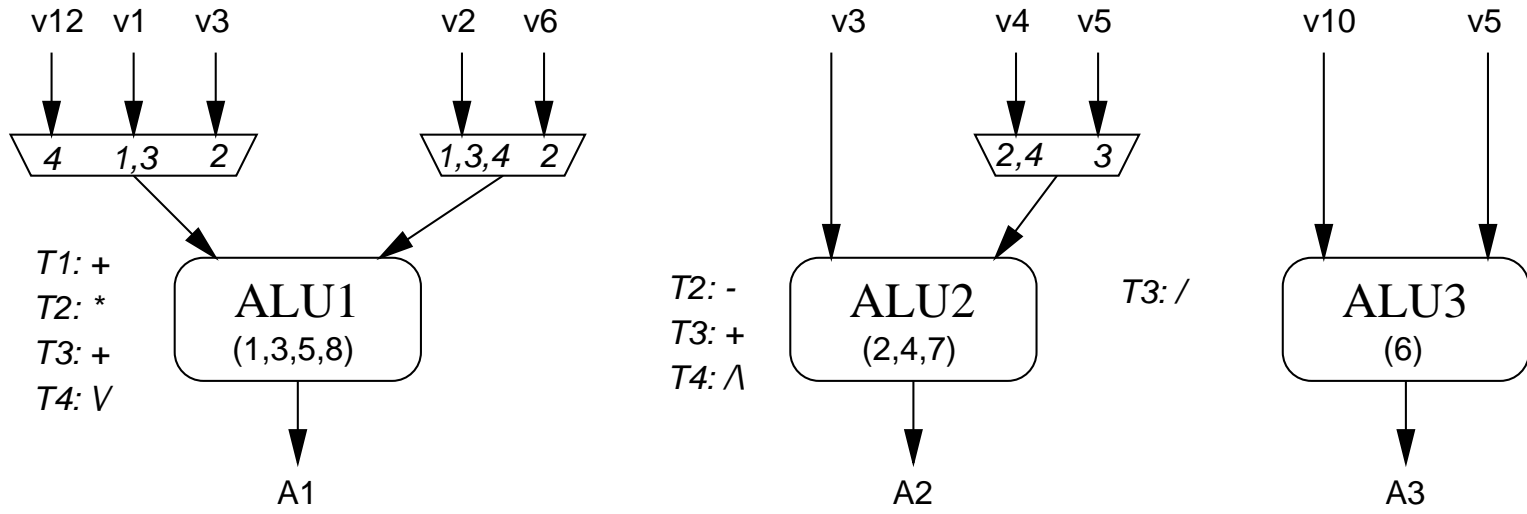

Allocation 8: Multiplexers optimized

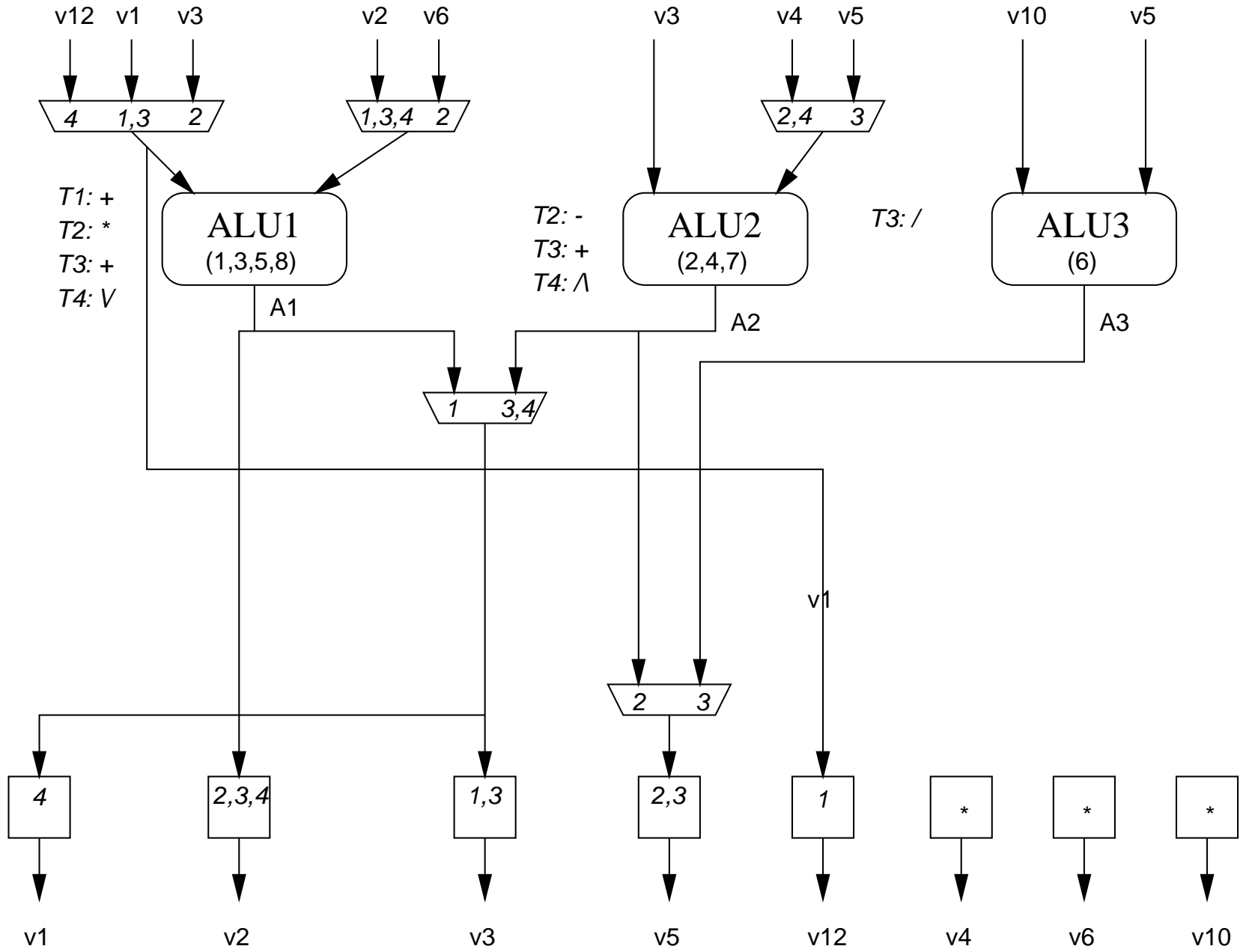

Allocation 9: Interconnections optimized (?)

Example Behavior

$$V3 = V1 + V2$$

$$V5 = V3 - V4$$

$$V7 = V3 * V6$$

$$V8 = V3 + V5$$

$$V9 = V1 + V7$$

$$V11 = V10 / V5$$

$$V13 = V3$$

$$V12 = V1$$

$$V14 = V11 \text{ and } V8$$

$$V15 = V12 \text{ or } V9$$

$$V1 = V14$$

$$V2 = V15$$

Schedule - I

A schedule:

$$r3 = r1 + r2$$

$$r7 = r3 - r4$$

$$r2 = r3 * r5$$

$$r3 = r3 + r7$$

$$r2 = r1 + r2$$

$$r7 = r6 / r7$$

$$r1 = r3 \text{ and } r7$$


$$r2 = r2 \text{ or } r8$$

$$r8 = r1$$

V1 to V15 merged into **r1 to r8**

Datapath - I

ALU performs +, -, *, /, and, or

 

$r3 = r1 + r2$
 $r7 = r3 - r4$
 $r2 = r3 * r5$
 $r3 = r3 + r7$
 $r2 = r1 + r2$
 $r7 = r6 / r7$
 $r1 = r3 \text{ and } r7$
 $r2 = r2 \text{ or } r8$

$r8 = r1$

Controller - I

Controller:

0	S0	S0	NOP	0000000000000000
1	S0	S1	NOP	0000000000000000
-	S1	S2	ADD	1111010010000010
-	S2	S3	SUB	1110000101000100
-	S3	S4	MUL	...
-	S4	S5	ADD	...
-	S5	S6	ADD	
-	S6	S7	DIV	
-	S7	S8	AND	
-	S8	S0	OR	...

Schedule and Datapath - II

$$r3 = r1 + r2$$

$$r8 = r1$$

$$r5 = r3 - r4$$

$$r2 = r3 * r6$$


$$r3 = r3 + r5$$

$$r5 = r5 * r7$$

$$r2 = r1 \text{ and } r2$$

$$r1 = r3 \text{ or } r5$$

$$r2 = r8 + r2$$

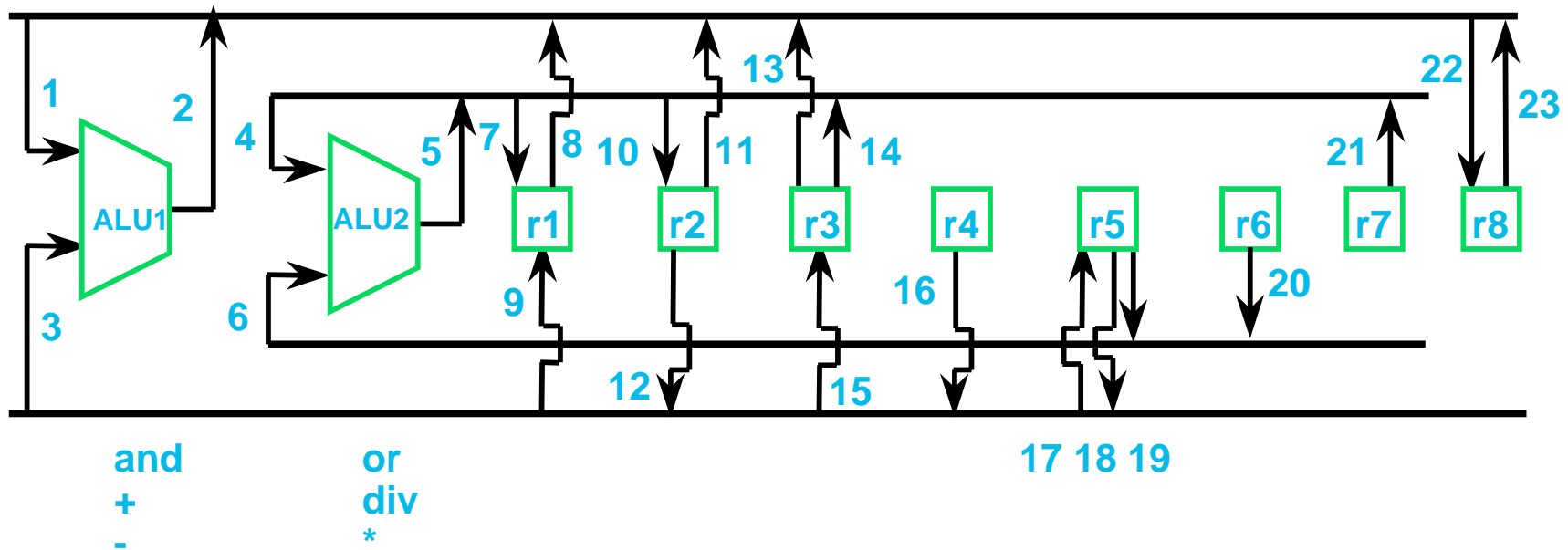

Controller - II

Controller

0	S0	S0	NOP	NOP	000000000000000000000000
1	S0	S1	NOP	NOP	000000000000000000000000
-	S1	S2	ADD	NOP	11100001000100100000010
-	S2	S3	SUB	MUL	...
-	S3	S4	ADD	DIV	...
-	S4	S5	AND	OR	
-	S5	S6	ADD	NOP	...